

# Multiple stage amplifiers

## *Aims:*

- *Examine a few common 2-transistor amplifiers:*
  - *Differential amplifiers*
  - *Cascode amplifiers*
  - *Darlington pairs*
  - *current mirrors*
- *Introduce formal methods for exactly analysing multiple stage amplifiers*



# Two stage BJT amplifiers

*We study them separately because they very often appear as building blocks. There are 9 possible cascades of 2 single stage transistor amplifiers. We will study the shaded ones.*

Name	BJT		Comments
	1st Stg	2nd Stg	
(voltage amp)	CE	CE	High Voltage gain
cascode	CE	CB	High bandwidth
(op-amp)	CE	CC	High $Z_{in}$ low $Z_{out}$
(current buffer)	CB	CE	Higher $Z_{out}$ than CB/CG
(current buffer)	CB	CB	Second stage to improve on CB/CG
(Not common)	CB	CC	Not common
(Not common)	CC	CE	Instead of CE, offers higher $Z_{in}$
differential amp	CC	CB	High voltage gain and bandwidth
darlington	CC	CC	High current gain

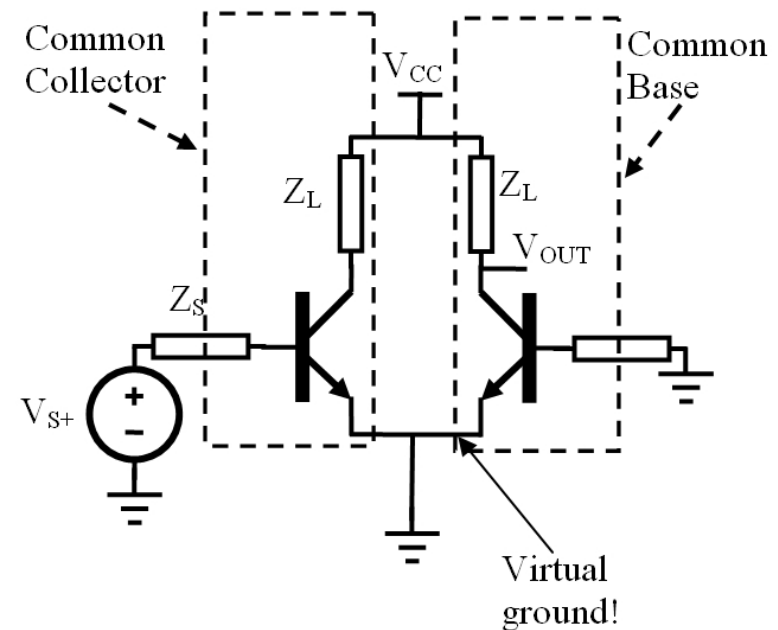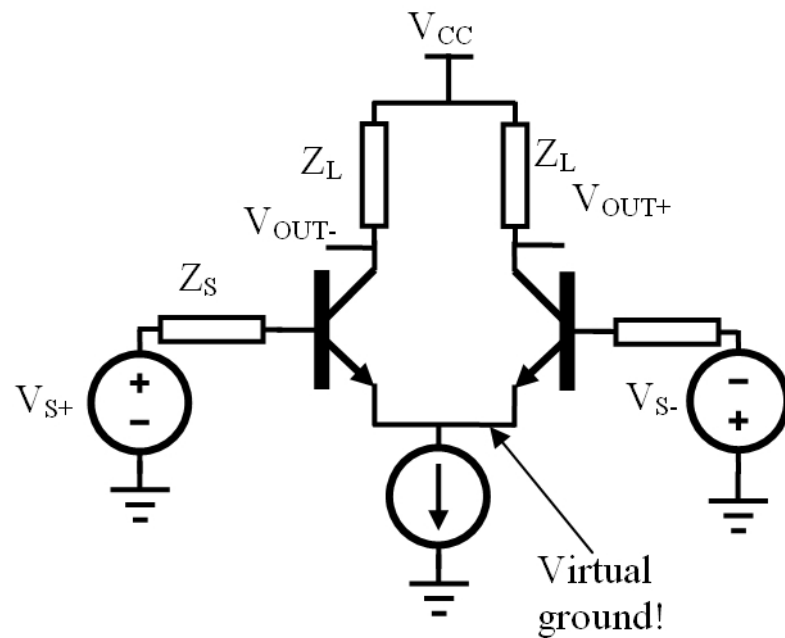
# Differential amplifier

- Half circuit (i.e. driven from one side) is CC followed by CB
- Very wide frequency response
- Extremely high voltage gain




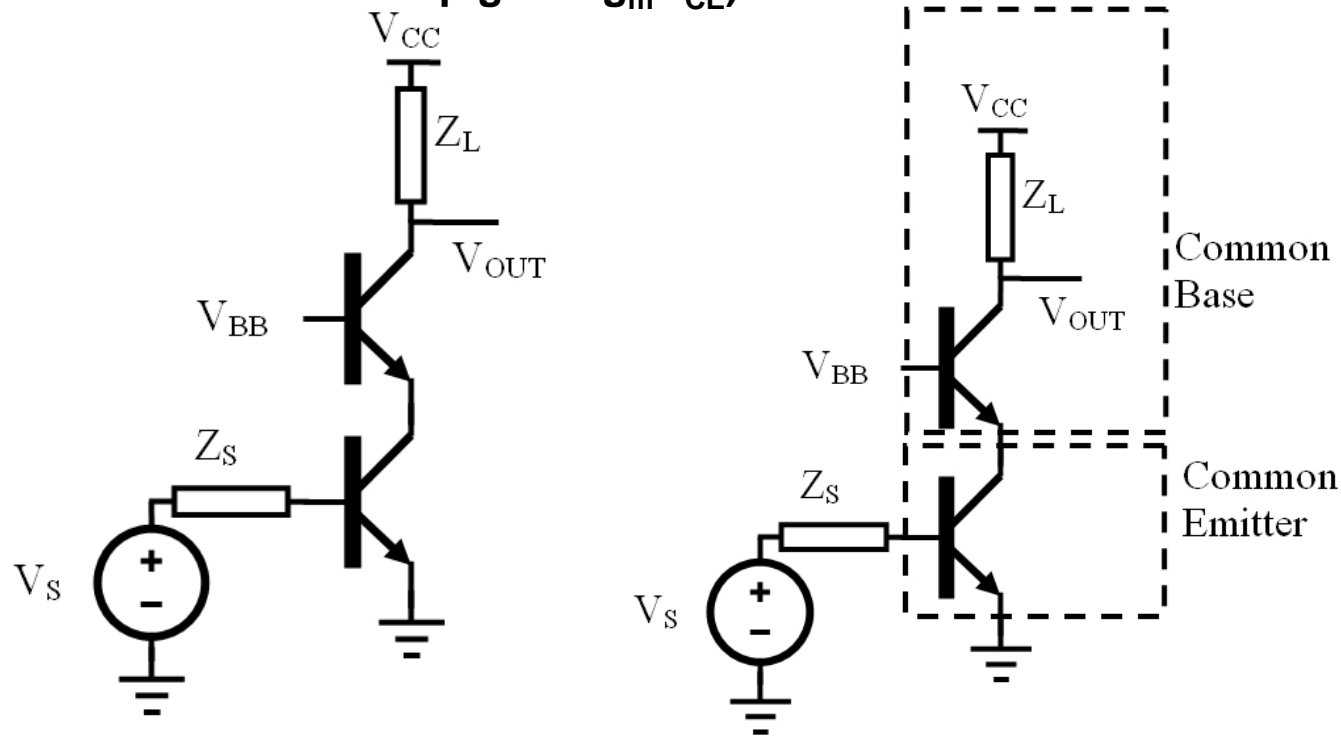
# Cascode amplifier

- Wideband voltage amplifier
- CE stage operates at gain=-1, minimising miller loading of input.
- CB gives all the voltage gain, acting as transimpedance of value  $Z_L$
- The cascode has a much higher output impedance (other than  $Z_L$ ) than the CE amplifier (the common emitter Early resistance acts as series-series feedback to the common base with loop gain  $=g_m R_{CE}$ )



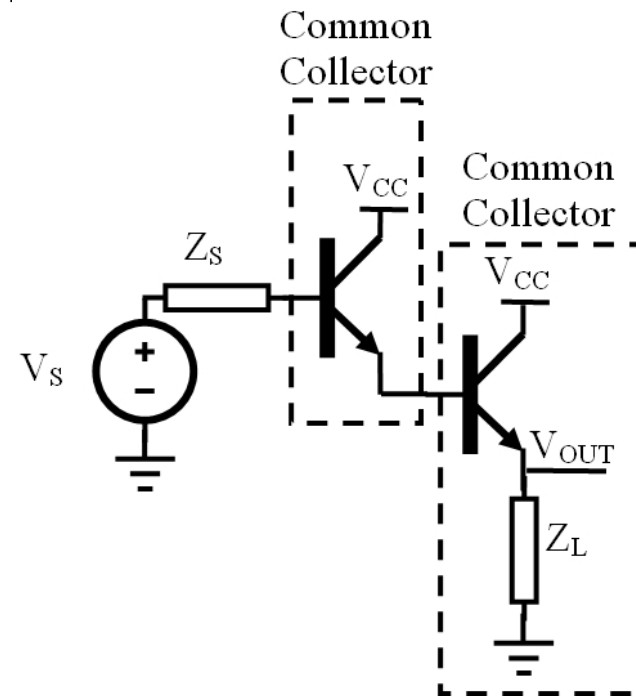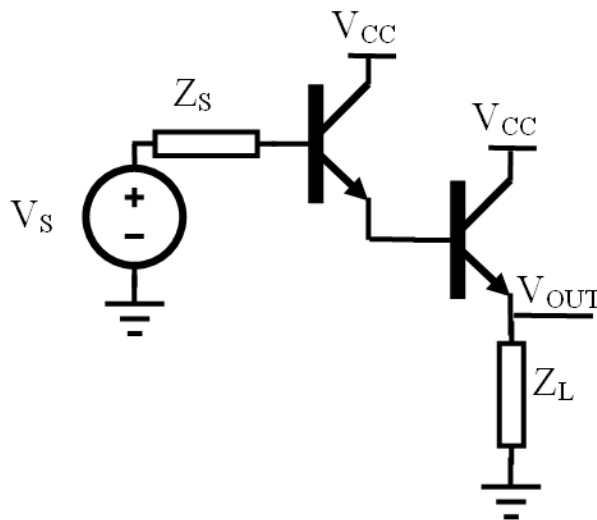
# Darlington pair

- The darlington pair is a high gain power amplifier it has:
  - *Unity voltage gain*
  - *High current gain equal to the product of the two transistor current gains*
- Often used as a single transistor for higher beta. But :
- has high input DC voltage drop
- Good frequency response due to the absence of shunt Miller feedback.
- However, series Miller feedback introduces driving capacitive loads.



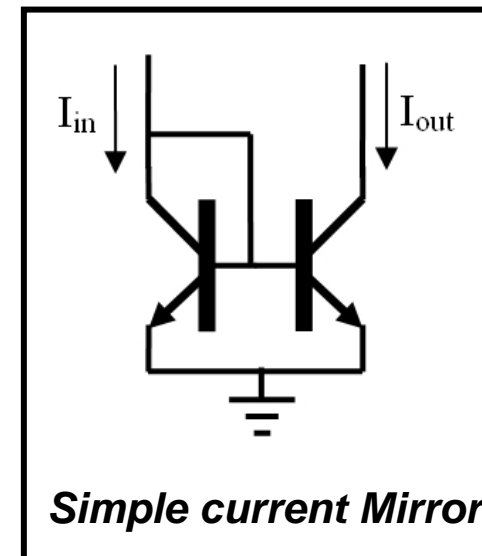
# Current mirrors

- Use one transistor with unity feedback as a transimpedance amplifier to measure the  $V_{BE}$  required for a given current.
- Use a second transistor as transconductor to create a copy of the input current
- Can make a current amplifier by using larger output transistor.
- Current gain is in error due to base currents (i.e finite current gain)
- No DC gain error in FET mirrors (remember the AC current gain of a FET scales as the inverse of frequency!)
- Main source of error transistor mismatch
  - *“ $V_{BE}$  mismatch at a constant current” (BJT)*
  - *$V_T$  mismatch in FET*
- AC analysis as in CE amplifier with extra source admittance due to input transistor
- Current mirrors are used for DC biasing multi-stage amplifiers
- Current mirrors often used load to a differential amplifier to turn the differential amplifier into a differential transconductor.




# Improved current mirrors

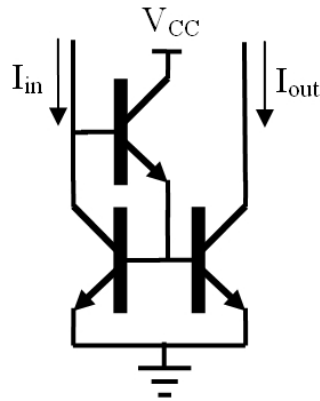

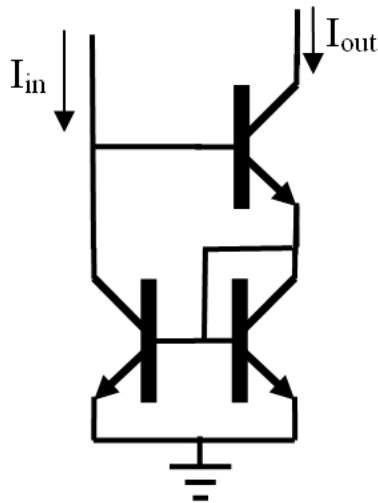
## The buffered mirror

The CC amplifier feeding the bases reduces current gain error



**The Wilson Mirror** has high output  $Z$ , since output stage is a cascode amplifier


# Scaling Mirrors: The Widlar mirror

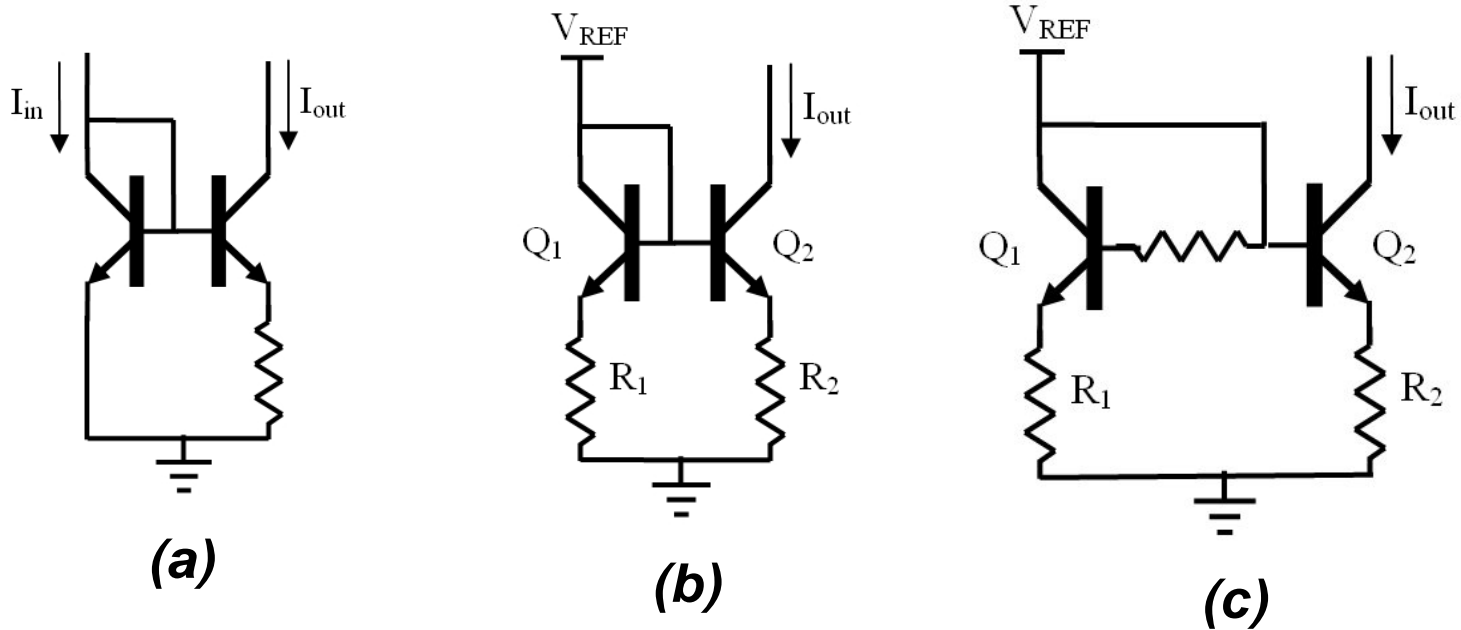


- The Widlar scaling mirror is often used as fixed scaling current source (a)
- Can be made as a buffered or a Wilson source (c)
- A feedback resistor can be added on the input side turning it into a transconductor (b)
- A base resistor as shown can provide “beta compensation” (i.e. introduce a zero in the frequency response (c)



## Some more mirrors

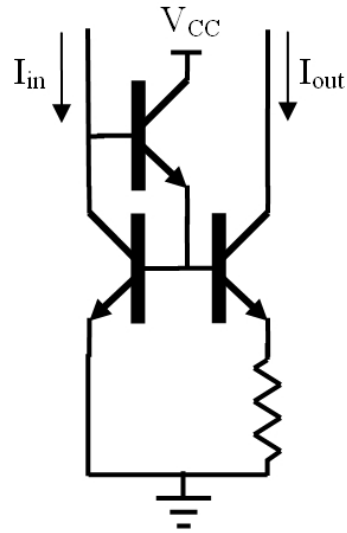

(a)

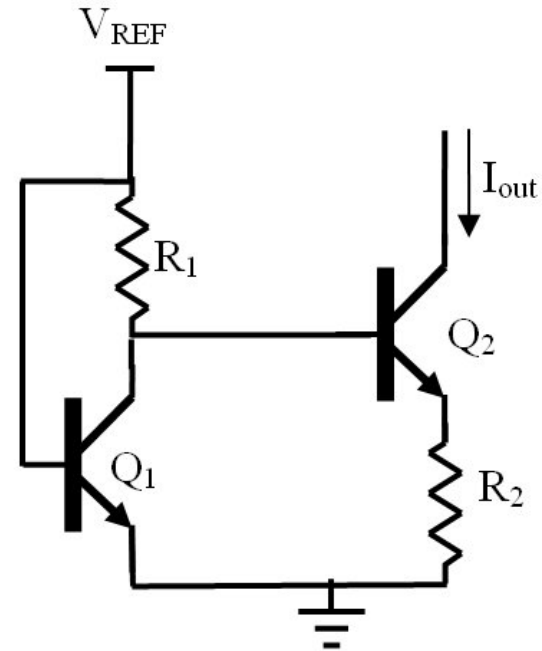


(b)

(a) *Buffered Widlar mirror*

(b) *The “gm-compensated” mirror*
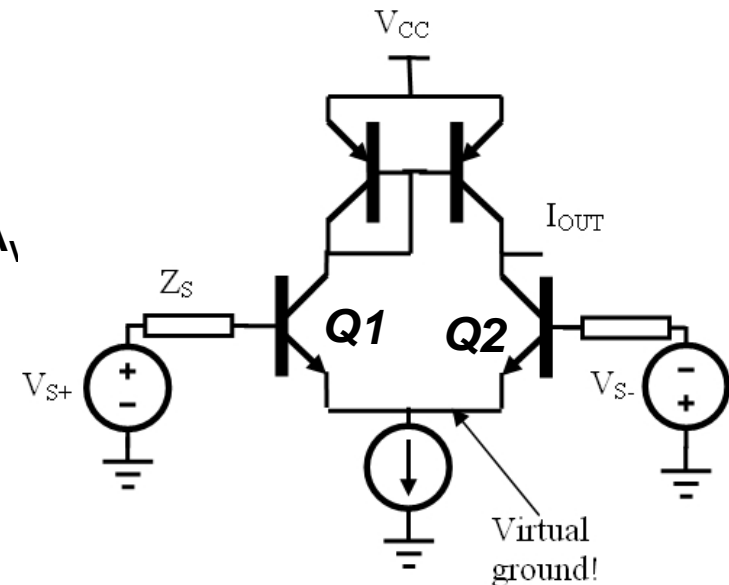
# Current mirror as a differential amp load

- The current mirror maps the left side current differential into the right side.
- The large signal response of this circuit is  $V_{out} = \tanh(V_+ - V_-)$
- This circuit (a 3 stage amplifier! Why?)
- This circuit It has extremely high voltage gain:  $A_v$  of the order of  $V_A/V_{th}$
- This circuit is also used for mixers if a transconductor is used in the place of the tail current source.
- There is no Miller effect on the left half circuit
- If this circuit drives a current sink at the output there is no Miller effect on the right half circuit either!
- The diff-amp has an extremely wide frequency response. This is partly a consequence of the resistive impedance match between the output of the first stage (emitter of Q1) and input of the second stage (emitter of Q2).




# Two stage FET amplifiers

- **The analogy we observed between single stage BJT and FET amplifiers applies, to two stage amplifiers. The correspondence is, as before,  $E \rightarrow S$ ,  $B \rightarrow G$ ,  $C \rightarrow D$ .**
- **The behaviour of BJT and FET configurations is very similar, except for the difference on the input side of the small signal equivalent circuit.**
- **A very useful possibility opens up: Use a FET for one stage and a BJT for the other. Mixed bipolar-FET two-stage combinations try to exploit the smaller input admittance of FETs and the better frequency response and power handling capability of bipolars at the same time.**
- **This approach gives rise to the “BiCMOS” manufacturing technologies which use FETs for input stages and BJTs for output stages, especially line drivers.**

Name	FET		Comments
	1st Stg	2nd Stg	
(voltage amp)	CS	CS	High Voltage gain
cascode	CS	CG	High bandwidth
(op-amp)	CS	CD	High $Z_{in}$ low $Z_{out}$
(current buffer)	CG	CS	Higher $Z_{out}$ than CB/CG
(current buffer)	CG	CG	Second stage to improve on CB/CG
(Not common)	CG	CD	Not common
(Not common)	CD	CS	Instead of CE, offers higher $Z_{in}$
differential amp	CD	CG	High voltage gain and bandwidth
darlington	CD	CD	High current gain
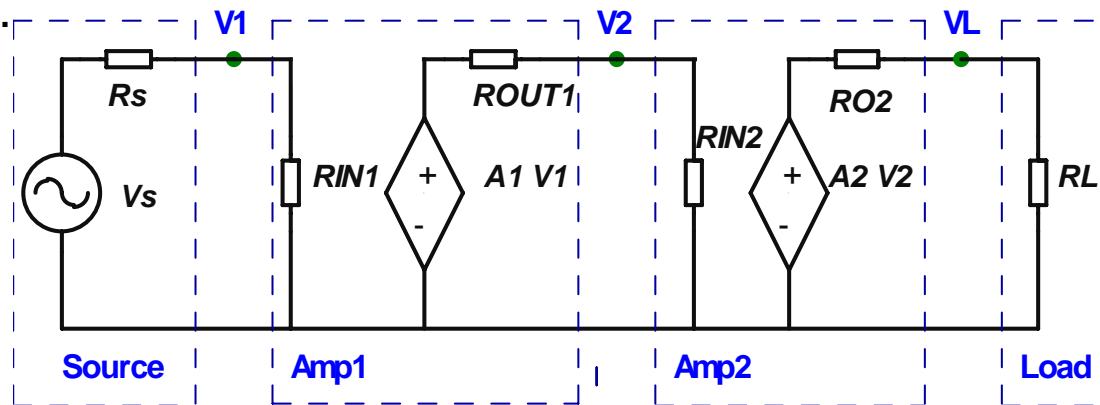
# Multistage amplifiers

- Multistage amplifiers are difficult to compute if the components are not unilateral.
- For unilateral amplifiers things are simple. We multiply gains with appropriate voltage dividers.



$$\frac{V_L}{V_s} = \frac{1}{1 + R_s Y_{in1}} A_1 \frac{1}{1 + R_{out1} Y_{in2}} A_2 \frac{1}{1 + R_{o2} Y_L}, \quad Y_x = \frac{1}{R_x}, \quad x \in \{in1, in2, L\}$$

- For non-unilateral amplifiers:
  - The input impedance of each stage depends on the input impedance of the next stage
  - The output impedance of each stage depends on the output impedance of the preceding stage.
- This problem has a solution but involves the solution of sets of simultaneous quadratic equations.

## Input - output impedance of a loaded amplifier

- We calculate the input impedance of a voltage amplifier driving a load  $Z_L$  :

$$\left. \begin{aligned} i_1 &= g_{11}v_1 + g_{12}i_2 \\ v_2 &= g_{21}v_1 + g_{22}i_2 \\ i_2 &= -v_2 Y_L \end{aligned} \right\} \Rightarrow \left. \begin{aligned} i_1 &= g_{11}v_1 - g_{12}Y_L v_2 \\ v_2 &= g_{21}v_1 - g_{22}Y_L v_2 \end{aligned} \right\} \Rightarrow$$


$$\left. \begin{aligned} g_{12}v_2 Y_L &= g_{11}v_1 - i_1 \\ (1 + g_{22}Y_L)v_2 &= g_{21}v_1 \end{aligned} \right\} \Rightarrow Z_{in} = \frac{v_1}{i_1} = \frac{1 + g_{22}Y_L}{g_{11} + \Delta_g Y_L}$$

- A similar calculation for the output impedance of a voltage amplifier driven by a finite impedance Thevenin source  $Z_S$  gives:

$$\left. \begin{aligned} i_1 &= g_{11}v_1 + g_{12}i_2 \\ v_2 &= g_{21}v_1 + g_{22}i_2 \\ v_1 &= v_s - i_1 Z_S \end{aligned} \right\} \Rightarrow \left. \begin{aligned} i_1 &= g_{11}(v_s - i_1 Z_S) + g_{12}i_2 \\ v_2 &= g_{21}(v_s - i_1 Z_S) + g_{22}i_2 \end{aligned} \right\} \Rightarrow$$

$$Z_{out} = dv_2 / di_2 = \frac{g_{22} + \Delta_g Z_S}{1 + g_{11}Z_S}$$
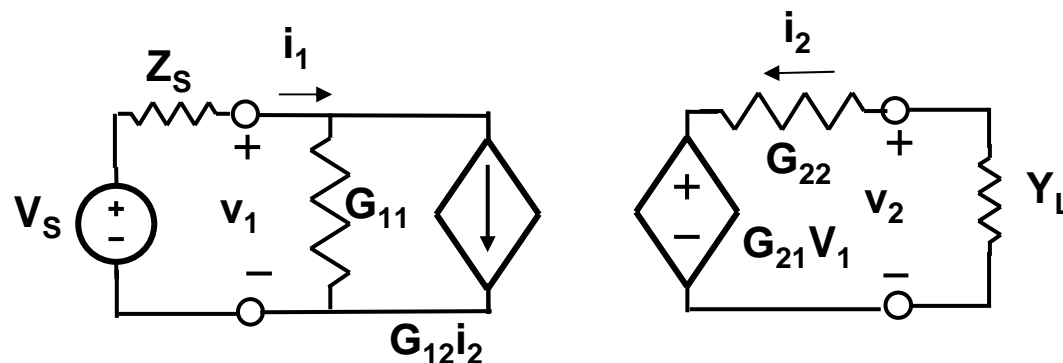
## Gain of a fully loaded voltage amplifier



We start with the amplifier definition, plus the source-load boundary conditions:

$$\begin{aligned} i_1 &= g_{11}v_1 + g_{12}i_2 \\ v_2 &= g_{21}v_1 + g_{22}i_2 \\ v_1 &= v_s - i_1 Z_s \\ i_2 &= -v_2 Y_L \end{aligned}$$

After some algebra we conclude that:

$$\frac{v_2}{v_s} = \frac{g_{21}}{(1 + g_{11}Z_s)(1 + g_{22}Y_L) - g_{12}g_{21}Z_s Y_L} = \frac{g_{21}}{1 + g_{11}Z_s + g_{22}Y_L + \Delta_g Y_L Z_s}, \quad \Delta_g = g_{11}g_{22} - g_{21}g_{12}$$

## Cascade connection: Transmission Parameters

In a cascade connection,


- $V_1$  of network  $X_2 = V_2$  of network  $X_1$
- $I_1$  of network  $X_2 = -I_2$  of network  $X_1$

We can define a new set of parameters so that we have a simple way to calculate the response of cascades of amplifiers.

A suitable definition is:

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

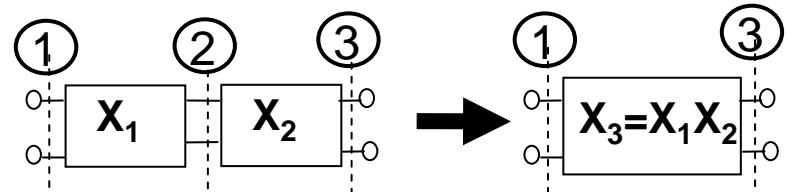With this definition, the ABCD parameters of a cascade of two networks are found from the matrix product of the individual ABCD matrices (ports labelled for clarity):



$$\left. \begin{aligned} \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} &= \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix} \\ \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix} &= \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_3 \\ -i_3 \end{bmatrix} \end{aligned} \right\} \Rightarrow \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_3 \\ -i_3 \end{bmatrix} \Rightarrow \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A_3 & B_3 \\ C_3 & D_3 \end{bmatrix} \begin{bmatrix} v_3 \\ -i_3 \end{bmatrix}$$

## Transmission (or ABCD) parameters (2)

The transmission matrix elements are related to the 4 gains:

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

$$A = \left. \frac{\partial v_1}{\partial v_2} \right|_{i_2=0} = \frac{1}{G_{21}} \quad B = \left. \frac{-\partial v_1}{\partial i_2} \right|_{v_2=0} = \frac{-1}{Y_{21}}$$

$$C = \left. \frac{\partial i_1}{\partial v_2} \right|_{i_2=0} = \frac{1}{Z_{21}} \quad D = \left. \frac{-\partial i_1}{\partial i_2} \right|_{v_2=0} = \frac{-1}{H_{21}}$$

A cascade of 2 amplifiers has gains:

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ C_1 A_2 + D_1 C_2 & C_1 B_2 + D_1 D_2 \end{bmatrix} \Rightarrow$$

$$g_f = \frac{1}{\frac{1}{g_{f1}g_{f2}} - \frac{1}{y_{f1}z_{f2}}} = \frac{g_{f1}g_{f2}y_{f1}z_{f2}}{y_{f1}z_{f2} - g_{f1}g_{f2}} \quad y_f = \frac{1}{\frac{1}{g_{f1}y_{f2}} - \frac{1}{y_{f1}h_{f2}}} = \frac{g_{f1}y_{f2}y_{f1}h_{f2}}{y_{f1}h_{f2} - g_{f1}y_{f2}}$$

$$z_f = \frac{1}{\frac{1}{z_{f1}g_{f2}} - \frac{1}{h_{f1}z_{f2}}} = \frac{z_{f1}g_{f2}h_{f1}z_{f2}}{h_{f1}z_{f2} - z_{f1}g_{f2}} \quad h_f = \frac{1}{\frac{1}{h_{f1}h_{f2}} - \frac{1}{z_{f1}y_{f2}}} = \frac{h_{f1}h_{f2}z_{f1}y_{f2}}{z_{f1}y_{f2} - h_{f1}h_{f2}}$$



## Transmission (or ABCD) parameters (3)

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

- **Note the sign of  $i_2$  and also the reverse sense of signal flow. The sign is chosen so the ABCD matrix of a cascade of two networks is just the matrix product of the individual ABCD matrices (compare this to the messy loading calculation before!)**
- **The reverse sense of signal flow is to keep the matrix finite if an amplifier is unilateral.**
- **The conversion from, say,  $Y$  to ABCD follows the same logic as the  $Y(H)$  calculation:**


$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 \\ Y_{11} & Y_{12} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 0 & 1 \\ -Y_{21} & -Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Rightarrow$$
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{-1}{Y_{21}} \begin{bmatrix} Y_{22} & 1 \\ \Delta_y & Y_{11} \end{bmatrix}, \Delta_y = Y_{11}Y_{22} - Y_{21}Y_{12}$$

**Remember that all ABCD parameters are inversely proportional to the gains. This is the reason for formally choosing port 2 as the input port.**


**The intuitive choice of input at port 1 would make all parameters inversely proportional to the reverse gains, which are small, and usually not very accurately determined.**
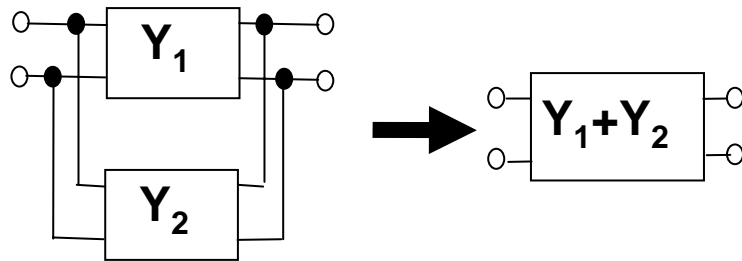
# Composition rules summary


For the exact calculation of circuit interconnections we can use 2-port matrix algebra:




**shunt-shunt: add Y matrices**

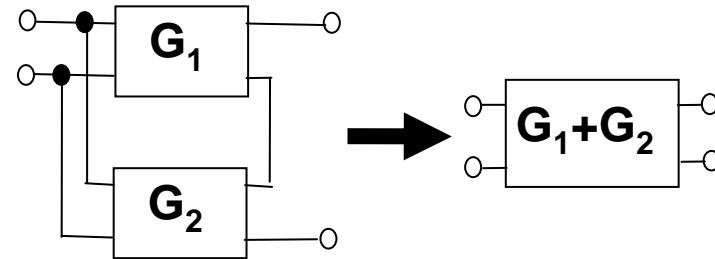


**shunt-series: add G matrices**

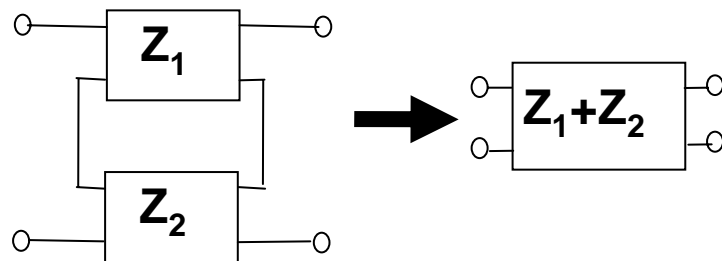

**series-series: add Z matrices**

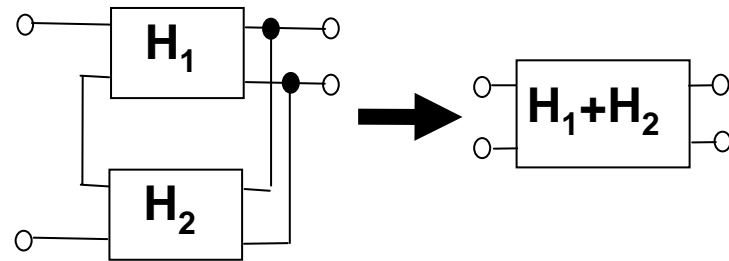

**series-shunt: add H matrices**

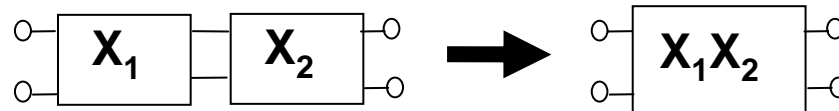

**cascade connection: multiply ABCD matrices**

## Multistage amplifiers: summary

- *Calculation of the response of unilateral multi-stage amplifiers is simple:*
  - *Product of gains and voltage dividers.*
- *Calculation of the response of non-unilateral multistage amplifiers involves determining for each stage:*
  - *the effect of source impedance on gain and output impedance*
  - *the effect of load impedance of input impedance and gain*
- *This typically leads to a set of simultaneous quadratic equations.*
- *A conceptually simpler analysis method involves the transmission or “ABCD” parameters which allow to describe all the loading effects of a non-unilateral cascade through a matrix product.*
- *With the introduction of ABCD parameters we have introduced simple ways to describe any connection between 2-port circuits.*