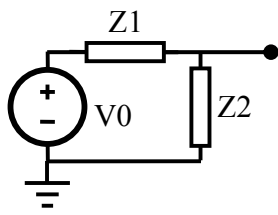


**E2.2 Analogue electronics**  
**Problem sheet 1 - ANSWERS**

**Q1.** Calculate the Thevenin and Norton equivalent circuits of the voltage divider circuit for all the component combinations shown in the table:

	V0	Z1	Z2
	DC	Resistor	Resistor
	AC	Resistor	Capacitor
		Capacitor	Resistor
		Resistor	Inductor
		Inductor	Capacitor

**ANSWER:** Turn source off to find:  $Z_T = \frac{1}{Y_N} = Z_1 // Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$

The open circuit voltage is the Thevenin voltage:  $V_T = V_0 \frac{Z_2}{Z_1 + Z_2}$

The Norton current is the short circuit current, i.e.:  $I_N = \frac{V_T}{Z_T} = \frac{V_0}{Z_1}$

The cases given:

V0	Z1	Z2	$V_T$	$Z_T = 1/Y_N$	$I_N$
DC	Resistor	Resistor	$\frac{V_0 Z_2}{Z_1 + Z_2}$	$\frac{R_1 R_2}{R_1 + R_2}$	$\frac{V_0}{Z_1}$
AC	Resistor	Capacitor	$\frac{V_0}{1 + j\omega R_1 C}$	$\frac{R_1}{1 + j\omega R_1 C}$	$\frac{V_0}{R_1}$
	Capacitor	Resistor	$\frac{j\omega C R_2 V_0}{1 + j\omega R_2 C}$	$\frac{R_2}{1 + j\omega R_2 C}$	$V_0 j\omega C$
	Resistor	Inductor	$\frac{V_0 j\omega L}{R_1 + j\omega L}$	$\frac{j\omega L R_1}{R_1 + j\omega L}$	$\frac{V_0}{R_1}$
	Inductor	Capacitor	$\frac{V_0}{1 - \omega^2 LC}$	$\frac{j\omega L}{1 - \omega^2 LC}$	$\frac{V_0}{j\omega L}$

**Q2.** Repeat Q1 but with a current source connected in the place of the voltage source.

**ANSWER:** The impedance Z1 is connected in series to a current source, so it is irrelevant. The Norton equivalent is just the source with Z2.

**Q3.** Calculate the small signal and the large signal Thevenin and Norton Equivalent circuits of a diode biased with a DC current of 1mA. The saturation current is 1fA. The thermal voltage is 25mV (at 17C)

**ANSWER:**

Large signal model:

The voltage developed on the diode with 1mA flowing is:

$$V_D = \frac{kT}{q} \ln\left(\frac{I_D}{I_0}\right) = 25mV \cdot \ln(10^{12}) = 25mV \cdot 27.6 \approx 0.69V$$

This is also the large signal Thevenin voltage.

The short circuit current is clearly 1mA.

So the large signal equivalent is:

$$V_T = 0.69V, I_N = 1mA, Z_T = 690\Omega$$

The small signal equivalent is again  $V_T = V_{OC} = 0.69V$

The small signal Thevenin resistance is quite different than the large signal Thevenin resistance:

$$Y_N = \frac{\partial I_D}{\partial V_D} = \frac{\partial(I_0 e^{qV_D/kT})}{\partial V_D} = \frac{I_D}{V_T} = \frac{1mA}{25mV} = 40\Omega$$

The Norton current has to be (for consistency!)

$$I_N = \frac{V_T}{Z_T} = \frac{0.69}{40} = 17.25mA$$

This is the case where the small and large signal Thevenin models are quite different!

**Q4.** A series connection of a diode and a  $1k\Omega$  resistor embedded in a big circuit develops 1V DC across it. Calculate the small signal Thevenin resistance of the resistor-diode connection. The diode saturation current is 1fA. The thermal voltage is 25mV (at 17C) (Do not include the voltage source in the calculation, only the diode and the resistor!)

**ANSWER**

We need to find the voltage and current developed on the diode. So we need to solve:

$$\underbrace{I_D R}_A + \underbrace{\frac{kT}{q} \ln\left(\frac{I_D}{I_0}\right)}_B = 1V$$

This can be done, for example, by iteration:

We assign the voltage B a starting value, eg  $B=0.5V$  then we compute  $A=0.5V$  and  $I = V_A / 1k\Omega$

We can then compute a new value for the B term:

$$V_B = \frac{kT}{q} \ln\left(\frac{I}{I_0}\right) \text{ and repeat until the two voltages converge}$$

This is done below:

Iteration	A	B	I
1	0.5	0.5	0.0005
2	0.326553	0.673447	0.000327
3	0.337204	0.662796	0.000337
4	0.336401	0.663599	0.000336
5	0.336461	0.663539	0.000336

We can now calculate the small signal Thevenin impedance:

$$Z_T = 1k\Omega + \frac{25mV}{0.336mA} = 3972\Omega$$

**Q5.** In the circuit diagram above, assume both  $Z_1$  and  $Z_2$  are arbitrary complex impedances and  $V_0$  a sinusoidal source of amplitude  $V_0$  and at a frequency  $\omega$ .

1. Derive an expression for the average power  $P_{Z2}$  dissipated in  $Z_2$ .
2. Derive also an expression for the average total power  $P_T$  delivered by the source  $V_0$  (which is the power dissipated in  $Z_1$  and  $Z_2$ )
3. What is the power delivered to  $Z_2$  if  $Z_1$  is finite and  $Z_2$  is zero?
4. What is the power delivered to  $Z_2$  if  $Z_1$  is finite and  $Z_2$  is infinite?
5. For what value of  $Z_2$  is  $P_{Z2}$  maximum, if  $Z_1$  is given? What is the maximum fraction of  $P_T$  that can be delivered to the load?

**ANSWER:**

$$a) \langle P_{Z2} \rangle = \langle \text{Re } IV_{Z2}^* \rangle = \langle |I|^2 \rangle \text{Re } Z_2 = \langle |V|^2 \rangle \frac{R_2}{|Z_1 + Z_2|^2} = \langle |V|^2 \rangle \frac{R_2}{(R_1 + R_2)^2 + (X_1 + X_2)^2}$$

$$b) \langle P_T \rangle = \langle \text{Re } IV^* \rangle = \langle |I|^2 \rangle \text{Re}(Z_1 + Z_2) = \langle |V|^2 \rangle \frac{R_1 + R_2}{|Z_1 + Z_2|^2} = \langle |V|^2 \rangle \frac{R_1 + R_2}{(R_1 + R_2)^2 + (X_1 + X_2)^2}$$

c) zero ( $V_{Z2}=0$ )

d) zero ( $I_{Z2}=0$ )

e)

$$\text{maximum of } \langle P_{Z2} \rangle = \langle |V|^2 \rangle \frac{R_2}{(R_1 + R_2)^2 + (X_1 + X_2)^2} \text{ occurs if } X_2 = -X_1$$

Then the maximum of

$$\langle P_{Z2} \rangle = \langle |V|^2 \rangle \frac{R_2}{(R_1 + R_2)^2} \text{ occurs for}$$

$$\frac{\partial}{\partial R_2} \langle P_{Z2} \rangle = 0 \Rightarrow \langle |V|^2 \rangle \frac{\partial}{\partial R_2} \frac{R_2}{(R_1 + R_2)^2} = 0 \Rightarrow \langle |V|^2 \rangle \frac{R_1 - R_2}{(R_1 + R_2)^3} = 0 \Rightarrow R_1 = R_2$$

This is  $\frac{1}{2}$  of  $P_T$ .