

## E2.2 Analogue electronics

### Problem sheet 2 (Week 4)

**Q1:** Determine the following small signal model parameters of an NPN bipolar transistor biased connected as a Common Emitter amplifier and biased with a DC collector current of 1mA and 10mA. The transistor DC current gain is  $\beta = 200$  and the Early voltage is  $V_A = 100V$  :

- Transconductance  $g_m$
- Hybrid Pi input resistance  $R_\pi$
- Collector output resistance  $R_{CE}$

**Q2:** Repeat question 1 if the transistor is PNP but all its other specifications are the same with those of the NPN transistor in question 1.

**Q3:** Draw the small signal equivalent circuit for an NPN bipolar transistor, including capacitances. Label all components. Assume the transistor is properly biased, and is connected as a current amplifier: The emitter is grounded, the base is driven by a current source and the collector is connected to the power supply through a current meter.

Calculate the small signal current gain of this amplifier as a function of frequency. Express this gain as a function of the equivalent circuit elements. Calculate the current gain at low and at high frequencies. At what frequency does the current gain start being frequency dependent?

**Q4:** Determine the  $C_{BE}$  and  $C_{BC}$  of an NPN bipolar transistor which has an  $f_T = 1$  GHz at a bias current  $I_C = 1mA$  if  $C_{BE} = 9C_{BC}$ .

**Q5:** Draw a diagram of an NPN bipolar transistor connected as a common Emitter voltage amplifier. The base is driven by an ideal voltage source which includes a DC bias  $V_0$  so that the DC collector current is 1mA, and a small AC component  $v$  so that  $V_{BE} = V_0 + v$ .

- Choose a load resistance  $R_C$  so that the DC gain is 200
- Choose a DC Collector supply so that the collector has a symmetric maximum swing. The Saturation voltage is 0.2V

**Q6:** Use the Miller Theorem to calculate symbolically the input impedance of an inverting amplifier built with an op-amp whose open loop gain is  $G=10$ .

**Q7:** Draw a small signal model of the circuit in Question 5. Use the Miller Theorem to simplify the circuit. Assume that for this circuit the results of Question 4 are valid. Calculate the frequency response of the voltage gain of this amplifier in the following 2 cases:

- The signal source has a Thevenin impedance  $R_T = 0$
- The signal source has a Thevenin impedance  $R_T = 1$  k $\Omega$