

E2.2 Analogue electronics
Problem sheet 3 (Week 5)


Q1: (Tutorial question for Week 6/7)

- What is the difference between an ideal op-amp, an ideal voltage amplifier and a commercial op-amp?
- Write an expression for the input impedance of the inverting amplifier below if $R_1=1\text{k}$, $R_2=100\text{k}$, the op-amp has a DC gain $G=10^4$ and its dominant pole is at $f=1.59\text{Hz}$. Evaluate the input impedance of this circuit at $f=15.9\text{kHz}$. The op-amp has zero input conductance and output resistance.

The open loop gain of a “dominant pole amplifier” is given by $G(f) = \frac{G_{DC}}{1+s\tau} = \frac{G_{DC}}{1+s/\omega_0}$, with

G_{DC} the DC gain and $\omega_0 = 1/\tau$ the pole (also called the “break”) frequency.

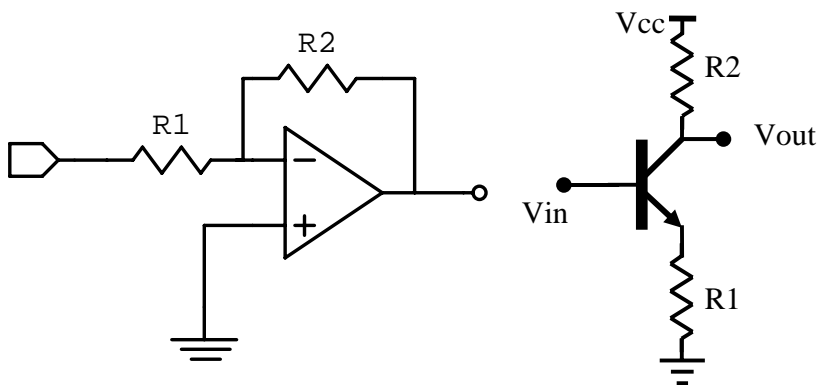- Calculate the DC voltage gain of the emitter degenerated common emitter amplifier below if $R_1=50\text{ Ohms}$, $R_2=200\text{ ohms}$ and $I_C=1\text{mA}$. (leave this item for week 6)



ANSWER:

- An ideal op-amp has infinite gain, zero input conductance, zero output resistance and zero reverse gain.
 An ideal voltage amplifiers has **finite** gain , zero input conductance, zero output resistance and zero reverse gain.
 A commercial op-amp has a large (but not infinite) gain, a small (but not zero) input conductance and output resistance. It also has negligibly small (but not zero) reverse current gain.
- The op-amp gain is: $G(\omega) = \frac{G_0}{1+j\omega/\omega_0}$ with $G_0 = 10^4$ and $\omega_0 = 10\text{ rad/s}$. Using the Miller

Theorem, the input impedance of this circuit is: $Z_{in} = R_1 + R_2 / \left(1 + \frac{G_0}{1+j\omega/\omega_0} \right)$.


$\omega_0 = 10\text{ rad/s}$.At $f=15.9\text{ krad/s}$, $\omega_0 = 10^5\text{ rad/s}$ and

$$Z_{in} = 1\text{ k}\Omega + 100\text{ k}\Omega / \left(1 + \frac{10^4}{1+j10^5/10^5} \right) = 1\text{ k}\Omega + 100\text{ k}\Omega / (1-j)$$

- f) The gain of the emitter degenerated amplifier is $G = -g_m' R_C$ where g_m' is the closed loop transconductance: $g_m' = \frac{-g_m}{1 + g_m R_E}$. At a 1 mA DC bias, and the resistor values given, $g_m = 40 \text{ mS} \Rightarrow g_m' = \frac{0.04}{1 + 0.04 \times 50} = 0.0133 \Rightarrow G = -2.66$. Please note that this is not equal to the ratio of $-R_2/R_1$, a useful approximation when $g_m R_E \gg 1$

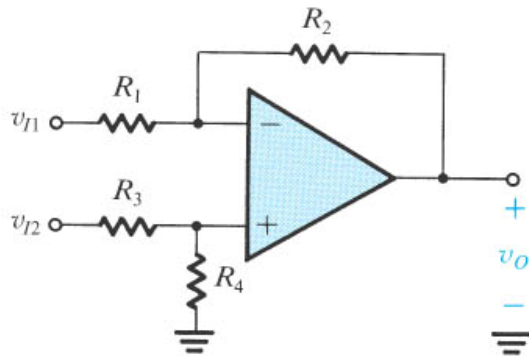Q2. Use superposition to show that the following circuit, built with an ideal op-amp, has an output equal to: $v_o = v_{i2} \left(\frac{1 + R_2/R_1}{1 + R_3/R_4} \right) - v_{i1} \frac{R_2}{R_1}$

Choose relative resistor values so that $v_{out} = A(v_{i1} - v_{i2})$. What is the value of the constant A?



ANSWER:

$$v_+ = \frac{R_4}{R_3 + R_4} v_{i2} = v_- = v_{i1} \frac{R_2}{R_1 + R_2} + v_o \frac{R_1}{R_1 + R_2} \Rightarrow v_o = \frac{R_1 + R_2}{R_1} \left(v_{i2} \frac{R_4}{R_3 + R_4} - v_{i1} \frac{R_2}{R_1 + R_2} \right)$$

$$v_o = v_{i2} \frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} - v_{i1} \frac{R_2}{R_1} \Rightarrow v_o = v_{i2} \left(\frac{1 + R_2/R_1}{1 + R_3/R_4} \right) - v_{i1} \frac{R_2}{R_1}$$

To prove we can get $v_{out} = A(v_{i1} - v_{i2})$ we need

$$\frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} = \frac{R_2}{R_1} \Rightarrow R_4 R_1 = R_2 R_3. \text{ The gain is simply } A = \frac{R_2}{R_1}$$


Q3: Apply the Miller Theorem to show that the input impedance of the following circuit is:

$Z_{in} = \frac{R}{1 - G}$. Derive an expression for the input impedance of this circuit if G is a dominant pole

inverting amplifier, the open loop gain of the amplifier is given by $G(f) = \frac{G_{DC}}{1+s\tau} = \frac{G_{DC}}{1+s/\omega_0}$.

What are the break frequencies of the impedance as a function of frequency? What is the input impedance at low frequencies and at very high frequencies?

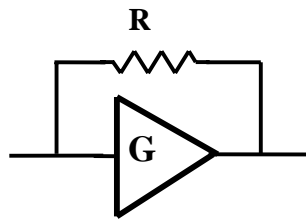The open loop gain of a “dominant pole amplifier” is given by $G(f) = \frac{G_{DC}}{1+s\tau} = \frac{G_{DC}}{1+s/\omega_0}$, with G_{DC} the DC gain and $\omega_0 = 1/\tau$ the pole (also called the “break”) frequency.



ANSWER:

$v_{out} = Gv_{in}$ Ohm’s law applies on R so that $i_R = \frac{v_{in} - v_{out}}{R} = \frac{(1-G)v_{in}}{R}$. This relation describes a resistor of value $Z_{in} = \frac{R}{1-G}$ as required. Alternatively, the answer is obtained by inspection, by applying the Miller theorem.

If G is an inverting dominant pole amplifier then,

$$Z_{in} = \frac{R}{1 + \frac{G_{DC}}{1+s\tau}} = R \frac{1+s\tau}{G_{DC} + 1 + s\tau} = \frac{R}{(G_{DC} + 1)} \frac{1+s\tau}{(1+s\tau/(1+G_{DC}))}$$


This impedance function has a zero at $f_z = \frac{1}{2\pi\tau}$ and a pole at $f_p = \frac{G_{DC} + 1}{2\pi\tau} = (G_{DC} + 1)f_z$

At low frequencies the impedance goes to $R/(G_{DC} + 1)$. At high frequencies it approaches R.

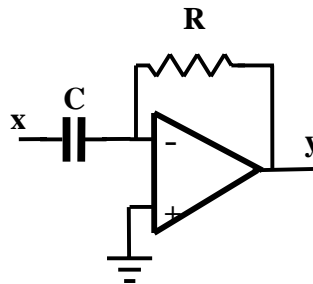Q4: Show that the transfer function of the ideal differentiator below constructed with a dominant pole amplifier is:


$$H(s) = \frac{v_{out}}{v_{in}} = \dots = \frac{-sRCG_{DC}}{s^2\tau RC + s(\tau + RC) + (G_{DC} + 1)}$$

Calculate the maximum gain of this filter which occurs roughly when denominator is purely imaginary.



ANSWER:

The inverting amplifier is modelled as

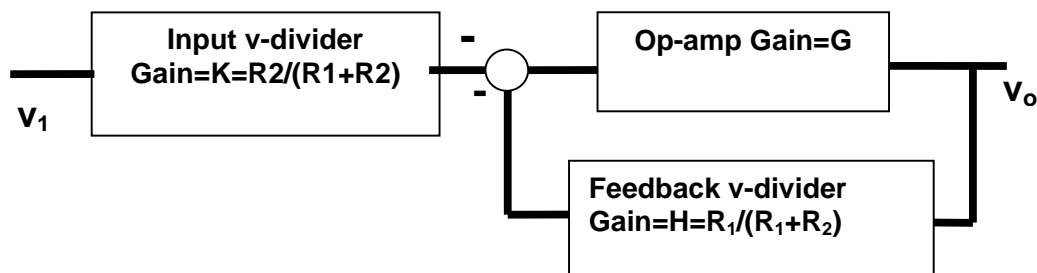

The block gains are

$$K = \frac{R}{R + 1/sC} = \frac{s\tau_0}{s\tau_0 + 1} \quad \text{and} \quad H = \frac{1/sC}{R + 1/sC} = \frac{1}{s\tau_0 + 1}, \quad \tau_0 = RC$$

The overall closed loop gain is

$$A_v = \frac{-KG}{1+GH} = \frac{-\frac{s\tau_0}{s\tau_0 + 1} \frac{G_{DC}}{1+s\tau}}{1 + \frac{1}{s\tau_0 + 1} \frac{G_{DC}}{1+s\tau}} = \frac{-s\tau_0 G_{DC}}{(s\tau + 1)(s\tau_0 + 1) + G_{DC}} = \frac{-s\tau_0 G_{DC}}{s^2\tau\tau_0 + s(\tau + \tau_0) + (G_{DC} + 1)} \quad \text{QED}$$

$$\text{Since } G(f) = \frac{G_{DC}}{1+s\tau} = \frac{G_{DC}}{1+s/\omega_0}$$

The maximum amplitude, which occurs near $s^2\tau\tau_0 + (G_{DC} + 1) = 0 \Rightarrow \omega_{\max} = \sqrt{\frac{G_{DC} + 1}{\tau\tau_0}}$, is

$$|A_{v\max}| = \frac{-\omega_{\max}\tau_0 G_{DC}}{\omega_{\max}(\tau + \tau_0)} = \frac{-\tau_0 G_{DC}}{(\tau + \tau_0)}$$