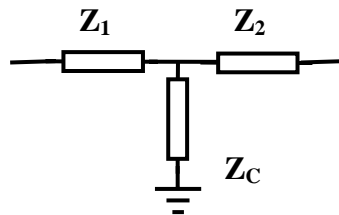


**E2.2 Analogue electronics**  
**Problem sheet 6 (Week 9)**

**Q1:** Show that the impedance matrix of the “Tee” circuit (shown below ) is:

$$Z_{TEE} = \begin{bmatrix} Z_1 + Z_C & Z_C \\ Z_C & Z_2 + Z_C \end{bmatrix}$$

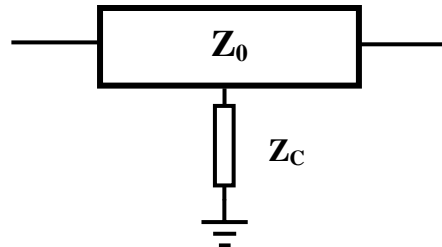


**Figure for problem 3:** The “tee” network

**Q2:** Show that the impedance matrix of a network consisting of a 2-port with impedance matrix

$$Z_0 = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \text{ and a impedance } Z_C \text{ along its common terminal connection is:}$$

$$Z' = \begin{bmatrix} z_{11} + Z_C & z_{12} + Z_C \\ z_{21} + Z_C & z_{22} + Z_C \end{bmatrix}$$

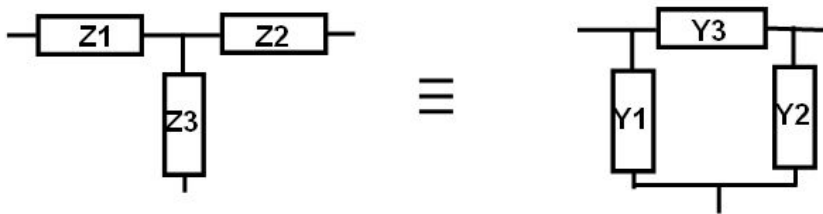


**Figure for problem 4:** Connecting an impedance along the common terminal of a 2-port.

**Q3:** Prove that the “Tee” and “Pi” networks are equivalent if:

$$Z_1 = \frac{Y_2}{Y_1 Y_2 + Y_2 Y_3 + Y_1 Y_3}, Z_2 = \frac{Y_1}{Y_1 Y_2 + Y_2 Y_3 + Y_1 Y_3}, Z_3 = \frac{Y_3}{Y_1 Y_2 + Y_2 Y_3 + Y_1 Y_3} \quad \text{or, equivalently, if}$$

$$Y_1 = \frac{Z_2}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}, Y_2 = \frac{Z_1}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}, Y_3 = \frac{Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}$$



**Figure for problem 5:** Equivalence of Tee and Pi networks

**Q4:** Given the Y-matrix for a network calculate its G-matrix

**Q5:** Given the G-matrix for a network calculate its Y-matrix

**Q6:** Use the results of Q4 and Q5 above to discover the exact form of the parallel form of the Miller theorem (what was shown in class was approximate!). What are the conditions for the approximation to be good?