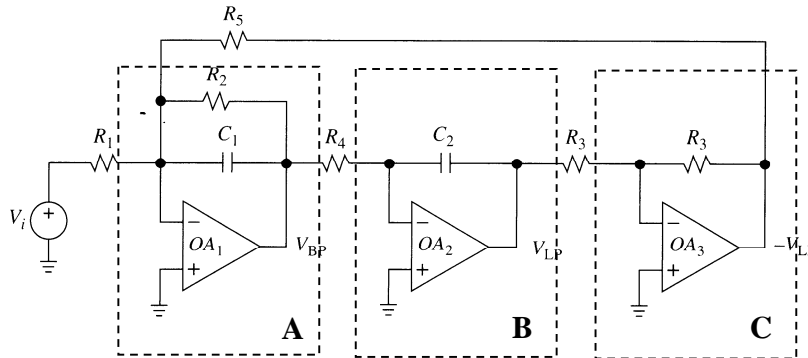


E2.2 Analogue electronics
Problem sheet 7 (Week 9)

Q1: (Tutorial question week 10/11)

Draw a flow graph for the biquadratic filter below, assuming the op-amps are ideal. Write an expression for the three transfer functions $G_{LP} = \frac{V_{LP}}{V_i}$, $G_{BP} = \frac{V_{BP}}{V_i}$ in terms of the block transimpedance gains and the connecting conductances.




ANSWER

Since the op-amps are ideal the networks in the shaded boxes are ideal transimpedance amplifiers of gains

$$Z_A = \frac{-R_2}{1 + sR_2C_1}, Z_B = \frac{-1}{sC_2}, Z_C = -R_3. \text{ The input terminals are virtual grounds, and sum currents .}$$

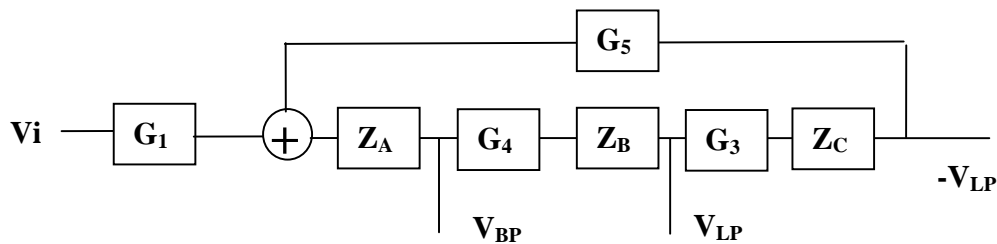Therefore, the flow graph can be drawn as:



With $G_n = 1/R_n$.

$$G_{BP} = \frac{V_{BP}}{V_i} = \frac{G_1 Z_A}{1 - Z_A G_4 Z_B G_3 Z_C G_5}$$

It follows that

$$G_{LP} = \frac{V_{LP}}{V_i} = \frac{G_1 Z_A G_4 Z_B}{1 - Z_A G_4 Z_B G_3 Z_C G_5} = G_{BP} G_4 Z_B$$

Q2. You are given the Common Emitter Y parameters of a Bipolar transistor. Calculate the Common Base H parameters of this transistor.

ANSWER:

Can be done directly, or in 2 steps, $Y_{CE} \rightarrow Y_{CB} \rightarrow H_{CB}$, or directly. We the second calculation, since the first is in the notes:

The voltages and currents in the two representations are related as:

$$i_{CB1} = i_E = -(i_B + i_C) = -i_{CE1} - i_{CE2}$$

$$i_{CB2} = i_C = i_{CE2}$$

$$v_{CB1} = v_{EB} = -v_{BE} = -v_{CE1}$$

$$v_{CB2} = v_{CB} = v_{CE} - v_{BE} = -v_{CE1} + v_{CE2}$$

We write the definition of the CB h matrix:

$$\begin{bmatrix} v_{CB1} \\ i_{CB2} \end{bmatrix} = h_{CB} \begin{bmatrix} i_{CB1} \\ v_{CB2} \end{bmatrix} \Rightarrow$$

$$\begin{bmatrix} -1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_{CE1} \\ v_{CE2} \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_{CE1} \\ i_{CE2} \end{bmatrix} = h_{CB} \left(\begin{bmatrix} 0 & 0 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} v_{CE1} \\ v_{CE2} \end{bmatrix} + \begin{bmatrix} -1 & -1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_{CE1} \\ i_{CE2} \end{bmatrix} \right) \Rightarrow$$

$$\begin{bmatrix} -1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_{CE1} \\ v_{CE2} \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix} y_{CE} \begin{bmatrix} v_{CE1} \\ v_{CE2} \end{bmatrix} = h_{CB} \left(\begin{bmatrix} 0 & 0 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} v_{CE1} \\ v_{CE2} \end{bmatrix} + \begin{bmatrix} -1 & -1 \\ 0 & 0 \end{bmatrix} y_{CE} \begin{bmatrix} v_{CE1} \\ v_{CE2} \end{bmatrix} \right) \Rightarrow$$

$$\begin{bmatrix} -1 & 0 \\ 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix} y_{CE} = h_{CB} \left(\begin{bmatrix} 0 & 0 \\ 1 & -1 \end{bmatrix} + \begin{bmatrix} -1 & -1 \\ 0 & 0 \end{bmatrix} y_{CE} \right) \Rightarrow$$

$$\begin{bmatrix} -1 & 0 \\ y_{21} & y_{22} \end{bmatrix} = h_{CB} \begin{bmatrix} -y_{11} - y_{21} & -y_{12} - y_{22} \\ 1 & -1 \end{bmatrix} \Rightarrow$$

$$h_{CB} = \begin{bmatrix} -1 & 0 \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} -y_{11} - y_{21} & -y_{12} - y_{22} \\ 1 & -1 \end{bmatrix}^{-1} = \frac{1}{(y_{11} + y_{12} + y_{21} + y_{22})} \begin{bmatrix} -1 & 0 \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} -1 & y_{12} + y_{22} \\ -1 & -y_{11} - y_{21} \end{bmatrix}$$

3. You are given the common source Y matrix of a FET. Compute its transmission matrix in common source configuration.

ANSWER:

The transmission matrix is:

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1/g_{21} & -1/y_{21} \\ 1/z_{21} & -1/h_{21} \end{bmatrix}$$

The y parameters are given. The rest are:

$$g_{21} = \frac{-y_{21}}{y_{22}}, z_{21} = \frac{-y_{21}}{\det y}, h_{21} = \frac{y_{21}}{y_{11}}$$


4. You are given the common source transmission matrix of a FET. Compute the common Gate and common Drain transmission matrices.

ANSWER

Same logic as Q2.

5. Solve the high pass sallen-key filter.

ANSWER:

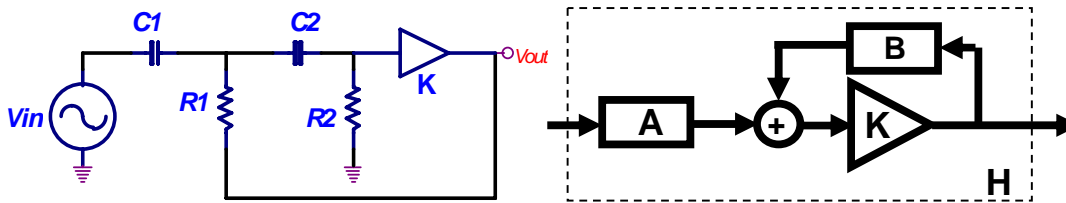

Derive A and B by superposition:

Convert V_{in} , C_1 , R_1 into a Thevenin equivalent: $V_T = \frac{sR_1C_1}{1 + sR_1C_1}$, $Z_T = \frac{R_1}{1 + sR_1C_1}$

And calculate the resultant voltage divider:

$$A = \frac{s^2 R_1 C_1 R_2 C_2}{s^2 R_1 C_1 R_2 C_2 + s(R_1 C_1 + R_2 C_2 + R_1 C_2) + 1} = \frac{s^2 \tau_1 \tau_2}{D}$$


$$B = \frac{s R_2 C_2}{s^2 R_1 C_1 R_2 C_2 + s(R_1 C_1 + R_2 C_2 + R_1 C_2) + 1} = \frac{s \tau_2}{D}$$

$$D = s^2 \tau_1 \tau_2 + s(\tau_1 + \tau_2 + \tau_{12}) + 1, \tau_1 = R_1 C_1, \tau_2 = R_2 C_2, \tau_{12} = R_1 C_2$$

$$H(s) = \frac{AK}{1 - BK} = \frac{s^2 \tau_1 \tau_2 K}{D - K s \tau_2} = \frac{s^2 \tau_1 \tau_2 K}{s^2 \tau_1 \tau_2 + s(\tau_1 + \tau_2(1 - K) + \tau_{12}) + 1}$$

6. Solve the Deliyannis-Friend All pass filter

ANSWER:

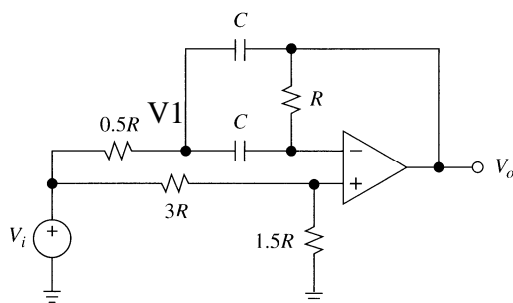

Evaluate the (3R, 1.5R) voltage divider to find that $V_- = V_+ = V_i / 3$

Write nodal equations:

At V_1 :

$$2G(V_i - V_1) + (V_o - V_1)sC + (V_- - V_1)sC = 0 \Rightarrow 2G(V_i - V_1) + (V_o - V_1)sC + (V_i/3 - V_1)sC = 0 \Rightarrow (2G + 2sC)V_1 - sCV_o = (2G + sC/3)V_i, \quad G = 1/R$$

At V_- :

$$sC(V_1 - V_-) + (V_o - V_-)G = 0 \Rightarrow sC(V_1 - V_i/3) + (V_o - V_i/3)G = 0 \Rightarrow sCV_1 + GV_o - (sC + G)V_i/3 = 0 \Rightarrow sCV_1 + GV_o = V_i(sC + G)/3$$

Put all together:

$$\begin{bmatrix} (2G + 2sC) & -sC \\ sC & G \end{bmatrix} \begin{bmatrix} V_1 \\ V_o \end{bmatrix} = \begin{bmatrix} 2G + sC/3 \\ (sC + G)/3 \end{bmatrix} V_i \Rightarrow \frac{V_o}{V_i} = \frac{G(2G + 2sC)(sC + G)/3 - sC(2G + sC/3)}{G(2G + 2sC) + s^2C^2}$$

Multiply numerator and denominator by $3R^2$ and call $\tau = RC$ to get:

$$\frac{V_o}{V_i} = \frac{1}{3} \frac{(2 + 2s\tau)(s\tau + 1) - s\tau(6 + s\tau)}{(2 + 2s\tau) + s^2\tau^2} = \frac{1}{3} \frac{s^2\tau^2 - 2s\tau + 2}{s^2\tau^2 + 2s\tau + 2}$$