

Large signal linearisation

Dynamic range is usually traded off for power

Usual solutions, reducing the Power-Dyn. range conflict:

- Feedback:
 - Series (emitter Degeneration)
 - Shunt (miller feedback)
- Interpolation
 - Connecting in parallel devices at different operating points
 - Connecting in parallel devices of different sizes
- Here we examine intrinsically large signal linear circuits
 - Dynamic translinear circuits **LOG DOMAIN filters**

Log Domain filters


Origins from audio use of compression to overcome noise
First papers in that context

A case of **E**xternally **L**inear, **I**nternally **N**on-linear circuits:



However, in bipolar transistors $I = \exp(V)$, so there is the possibility
an ELIN circuit is actually linear in the current mode!

The Adams Log domain filter

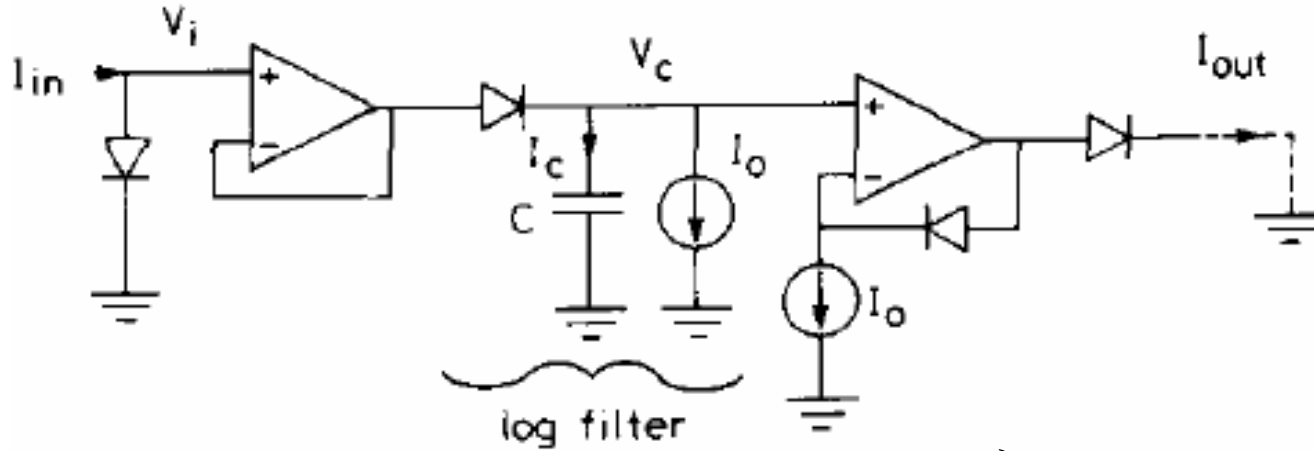

$$\left. \begin{aligned}
 I_{in} &= I_s e^{\beta V_i} \Rightarrow V_i = V_T \ln(I_i / I_s) \\
 I_C + I_0 &= C \frac{dV_C}{dt} + I_0 = I_s e^{\beta(V_i - V_C)} = I_{in} e^{-\beta V_C} \\
 I_{out} &= I_s e^{\beta V_1} = I_s e^{\beta V_C + \ln(I_0 / I_s)} = I_s e^{\beta V_C} I_0 / I_s = I_0 e^{\beta V_C}
 \end{aligned} \right\} \text{with } \beta = q / kT = 1 / V_T$$

$$\frac{dx}{dt} = \beta \frac{dV_C}{dt} x$$

$$C \frac{dV_C}{dt} + I_0 - I_{in} e^{-\beta V_C} = 0 \Rightarrow \frac{C}{\beta x} \frac{dx}{dt} + I_0 - \frac{I_{in}}{x} = 0 \Rightarrow \frac{C}{\beta} \frac{dx}{dt} + I_0 x = I_{in}$$

The Adams filter, continued

$$\frac{C}{\beta x} \frac{dx}{dt} + I_0 - \frac{I_{in}}{x} = 0 \Rightarrow \frac{C}{\beta} \frac{dx}{dt} + I_0 x = I_{in} \Rightarrow$$

$$\frac{dx}{dt} + \frac{\beta I_0}{C} x = \frac{\beta I_{in}}{C}$$

$$I_{out} = I_0 x$$

This is a first order low pass filter for x , with a Laplace space solution:

$$\frac{dI_{out}}{dt} + \frac{\beta}{C} I_0 I_{out} = \frac{\beta I_0 I_{in}}{C} \Rightarrow sX + \omega_0 X = \omega_0 U$$

$$\frac{X(s)}{U(s)} = \frac{\omega_0}{s + \omega_0}, \quad \omega_0 = \frac{\beta I_0}{C}$$

This is in a “state variable” form, so we examine state variable models next


State-variable Models

- Introduction
- Standard State-variable Format
- Advantages of State-variable Models
- Simulation Diagrams
- State-variable Models from Transfer Functions
- Transfer Functions from State-variable Models

Introduction

- We have already come across:
 - **linear differential equation models**
 - **transfer function models**
- We now consider the **state-variable model**, also called the **state-space model**.
- This is a differential equation model, but the equation is written in a specific format.
- The idea is that an n th order differential equation is decomposed into a set of n 1st order equations written in matrix-vector form.
- This decomposition is achieved by defining internal variables, called **states**, whose time evolution completely characterises the behaviour of the system.

Example

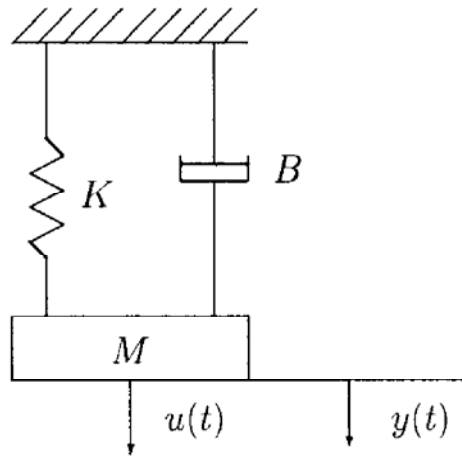

$$M\ddot{y}(t) + B\dot{y}(t) + Ky(t) = u(t)$$

- Define $x_1(t) = y(t)$, $x_2(t) = \dot{y}(t)$.

$$\Rightarrow \dot{x}_1(t) = x_2(t)$$

$$\Rightarrow \dot{x}_2(t) = -\frac{K}{M}x_1(t) - \frac{B}{M}x_2(t) + \frac{u(t)}{M}$$

or in matrix form:

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{K}{M} & -\frac{B}{M} \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{M} \end{bmatrix} u(t)$$

$$y(t) = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}$$

- This is an example of a **single input/single output** state-variable model.

Standard State-variable Format

- The state of a system at time t_1 is the amount of information at t_1 that, together with all inputs for $t \geq t_1$, uniquely determines the system behaviour for all $t \geq t_1$.
- State-variable models have the form:

$$\dot{x}(t) = Ax(t) + Bu(t) \quad (\text{state equation})$$

$$y(t) = Cx(t) + Du(t) \quad (\text{output equation})$$

$$x(0) = x_0 \quad (\text{initial condition})$$

where

$$A : n \times n \quad (\text{system matrix})$$

$$B : n \times r \quad (\text{input matrix})$$


$$C : p \times n \quad (\text{output matrix})$$

$$D : p \times r \quad (\text{direct feedthrough matrix})$$

$$x(t) : n \times 1 \quad (\text{state vector})$$

$$u(t) : r \times 1 \quad (\text{input vector})$$
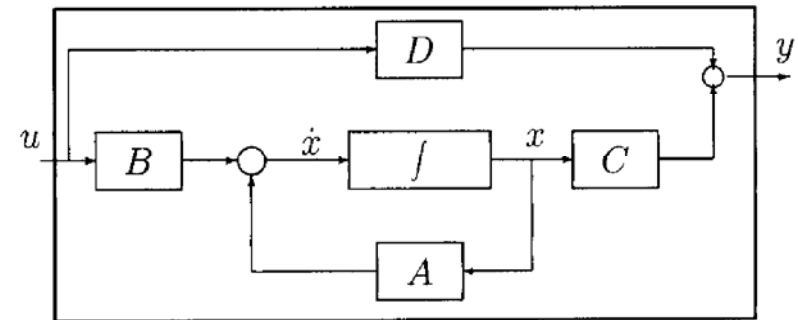
$$y(t) : p \times 1 \quad (\text{output vector})$$



Example

- Consider the coupled differential equations:

$$\begin{aligned}\ddot{y}_1 + k_1\dot{y}_1 + k_2y_1 &= u_1 + k_3u_2 \\ \dot{y}_2 + k_4y_2 + k_5\dot{y}_1 &= k_6u_1\end{aligned}$$

- Define: $x_1 = y_1$, $x_2 = \dot{y}_1$, $x_3 = y_2$

- This gives the state equations:

$$\begin{aligned}\dot{x}_1 &= x_2 \\ \dot{x}_2 &= -k_2x_1 - k_1x_2 + u_1 + k_3u_2 \\ \dot{x}_3 &= -k_5x_2 - k_4x_3 + k_6u_1\end{aligned}$$

and the output equations:

$$y_1 = x_1, \quad y_2 = x_3$$

- Collecting these into matrix form gives the 2-input 2-output state-variable model

$$\underbrace{\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 0 & 1 & 0 \\ -k_2 & -k_1 & 0 \\ 0 & -k_5 & -k_4 \end{bmatrix}}_A \underbrace{\begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}}_x + \underbrace{\begin{bmatrix} 0 & 0 \\ 1 & k_3 \\ k_6 & 0 \end{bmatrix}}_B \underbrace{\begin{bmatrix} u_1 \\ u_2 \end{bmatrix}}_u$$

$$\underbrace{\begin{bmatrix} y_1 \\ y_2 \end{bmatrix}}_y = \underbrace{\begin{bmatrix} 1 & 0 & 0 \\ 0 & 0 & 1 \end{bmatrix}}_C \underbrace{\begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix}}_x$$

Advantages of State-variable Models

- State-variable models give knowledge about the **internal structure** as well as the input-output characteristics of the system.
- There are **computational** advantages:
 - **time-domain** matrix methods lend themselves naturally to computer solution, especially for high order models.
 - matrix methods enable us to easily determine the **transient response** and evaluate the system performance.
- A good unified framework for several advanced control theories, such as **optimal control** design methods.
- A natural framework for system **simulation**.
- Extensions to:
 - **multivariable** systems
 - **nonlinear** systems
 - **time-varying** systemsare (relatively) straightforward.


Simulation Diagrams

- These are block diagrams (or signal flow graphs) that are constructed to have a given transfer function or to model a set of differential equations.
- There are three elements in a simulation diagram:
 - an **integrator** (whose transfer function is $\frac{1}{s}$)
 - a pure **gain**
 - a **summer**

All these components can be easily constructed using simple electronic devices.

- They are useful in constructing computer simulations (digital or analogue) of a given system.
- For the mass-spring system we have:
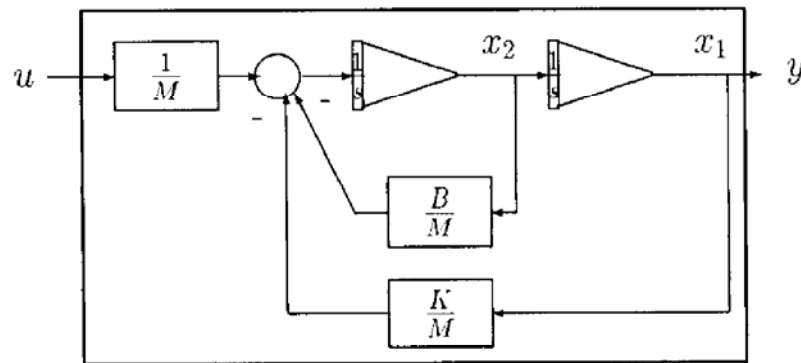
$$\begin{aligned}\dot{x}_1(t) &= x_2(t) \\ \dot{x}_2(t) &= -\frac{K}{M}x_1(t) - \frac{B}{M}x_2(t) + \frac{u(t)}{M}\end{aligned}$$



State-variable Models from Transfer Functions

- There are simulation diagrams which can be derived from general transfer functions of the form:

$$\frac{y(s)}{u(s)} = g(s) = \frac{b_{n-1}s^{n-1} + b_{n-2}s^{n-2} + \dots + b_0}{s^n + a_{n-1}s^{n-1} + a_{n-2}s^{n-2} + \dots + a_0}$$

- Divide numerator and denominator by s^n :

$$y(s) = \frac{b_{n-1}s^{-1} + b_{n-2}s^{-2} + \dots + b_0s^{-n}}{1 + a_{n-1}s^{-1} + a_{n-2}s^{-2} + \dots + a_0s^{-n}} u(s)$$

- Set

$$e(s) := \frac{u(s)}{1 + a_{n-1}s^{-1} + a_{n-2}s^{-2} + \dots + a_0s^{-n}}$$


so that

$$y(s) = [b_{n-1}s^{-1} + b_{n-2}s^{-2} + \dots + b_0s^{-n}] e(s)$$

- This gives


$$e(s) = u(s) - [a_{n-1}s^{-1} + a_{n-2}s^{-2} + \dots + a_0s^{-n}] e(s)$$

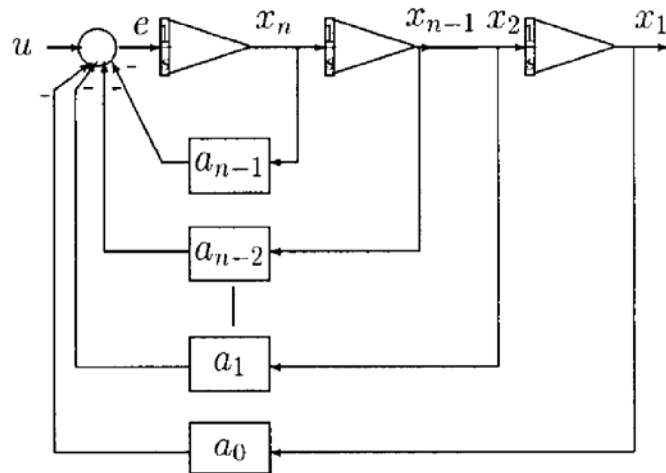- This has the following simulation diagram:



- Complete the diagram by setting
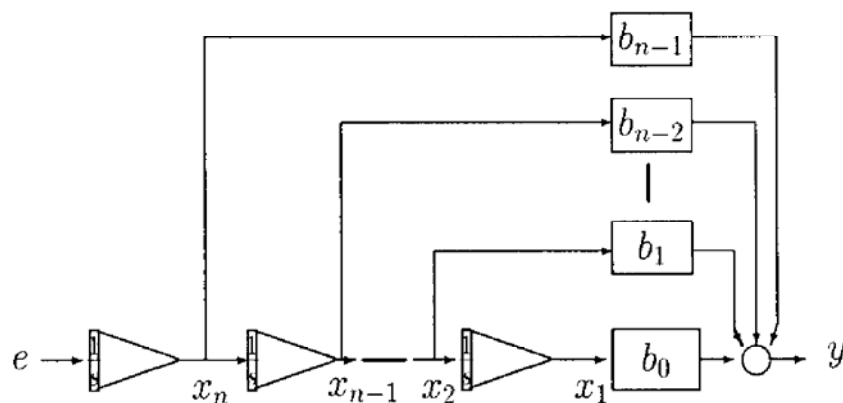
$$y(s) = [b_{n-1}s^{-1} + b_{n-2}s^{-2} + \dots + b_0s^{-n}] e(s)$$



- The state variables satisfy:

$$\begin{aligned} \dot{x}_1 &= x_2 \\ \dot{x}_2 &= x_3 \\ &\vdots \\ \dot{x}_{n-1} &= x_n \\ \dot{x}_n &= -a_0x_1 - a_1x_2 - \dots - a_{n-2}x_{n-1} \\ &\quad - a_{n-1}x_n + u \end{aligned}$$

while the output is

$$y = b_0x_1 + b_1x_2 + \dots + b_{n-2}x_{n-1} + b_{n-1}x_n$$

- In matrix form this yields the state-variable model:


$$\dot{x} = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 \\ 0 & 0 & 1 & \dots & 0 \\ \vdots & \vdots & \ddots & \ddots & 0 \\ 0 & 0 & \dots & 0 & 1 \\ -a_0 & -a_1 & \dots & -a_{n-2} & -a_{n-1} \end{bmatrix} x + \begin{bmatrix} 0 \\ 0 \\ \vdots \\ 0 \\ 1 \end{bmatrix} u$$

$$y = [b_0 \ b_1 \ \dots \ b_{n-2} \ b_{n-1}] x$$

- Note the direct connection with the coefficients of the transfer function:

$$g(s) = \frac{b_{n-1}s^{n-1} + b_{n-2}s^{n-2} + \dots + b_0}{s^n + a_{n-1}s^{n-1} + a_{n-2}s^{n-2} + \dots + a_0}$$

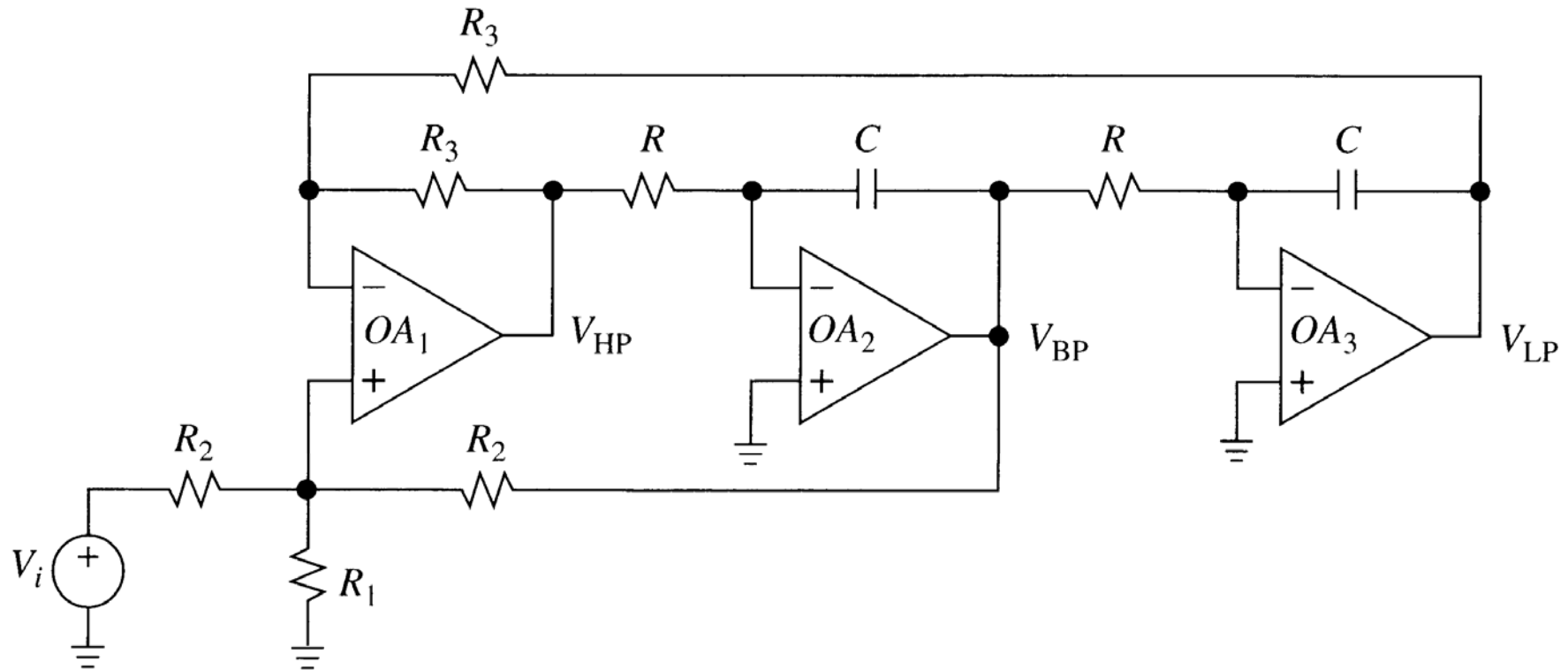
Example of voltage mode state variable filter: KHN




Observe the 3 possible outputs implementing low pass, band pass and high pass filters, demonstrating that each response is the derivative of the preceding one

Lossy state variable analysis: The Tow Thomas filter

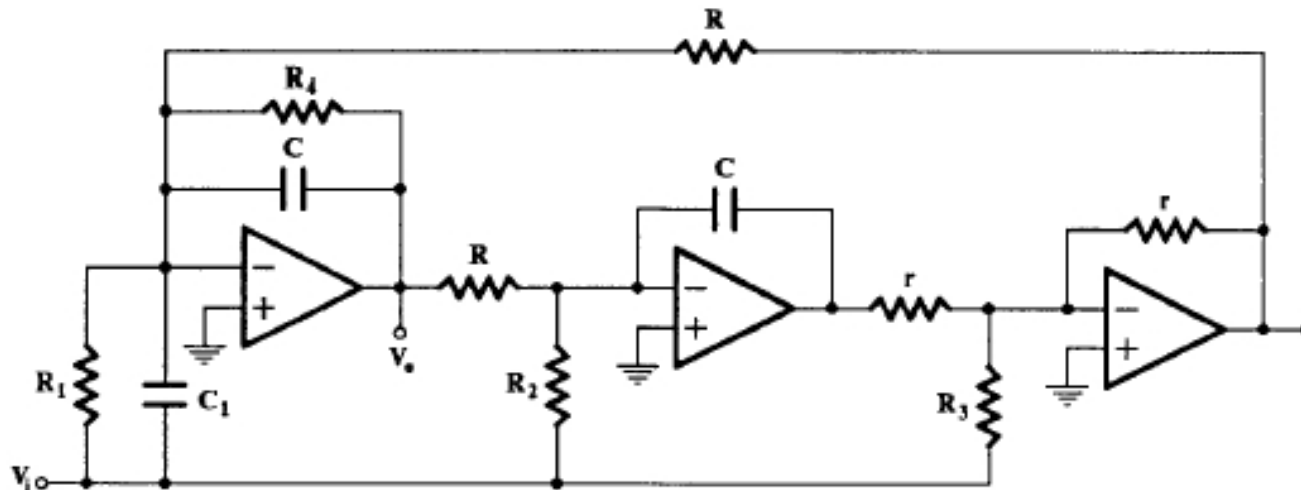- The state variable model is not unique. The decomposition can be slightly modified to work with lossy integrators (see Frey's paper)
- An example of a partial lossy decomposition is the Tow Thomas filter.




The Bernoulli cell

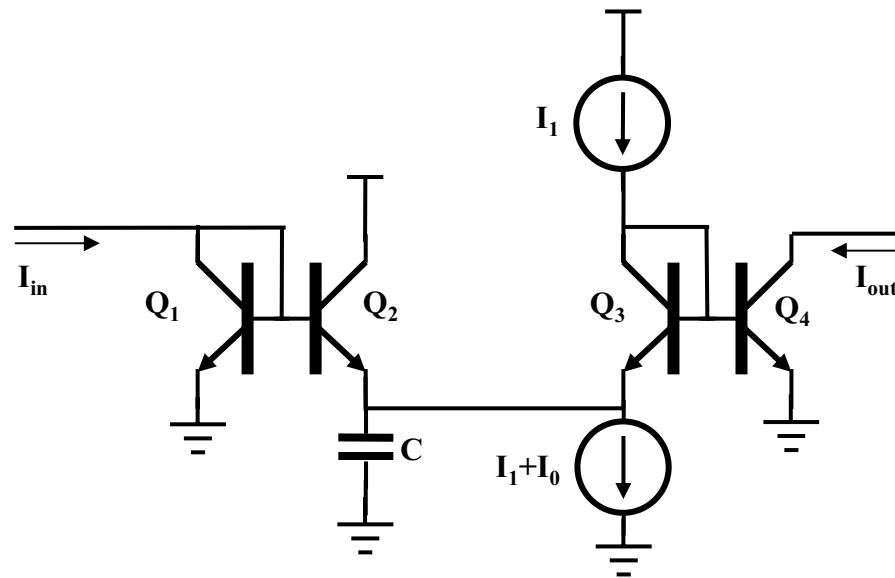


This is essentially the same circuit as the Adams circuit. Prove it!
If I_0 is very small this can implement an essentially ideal integrator.

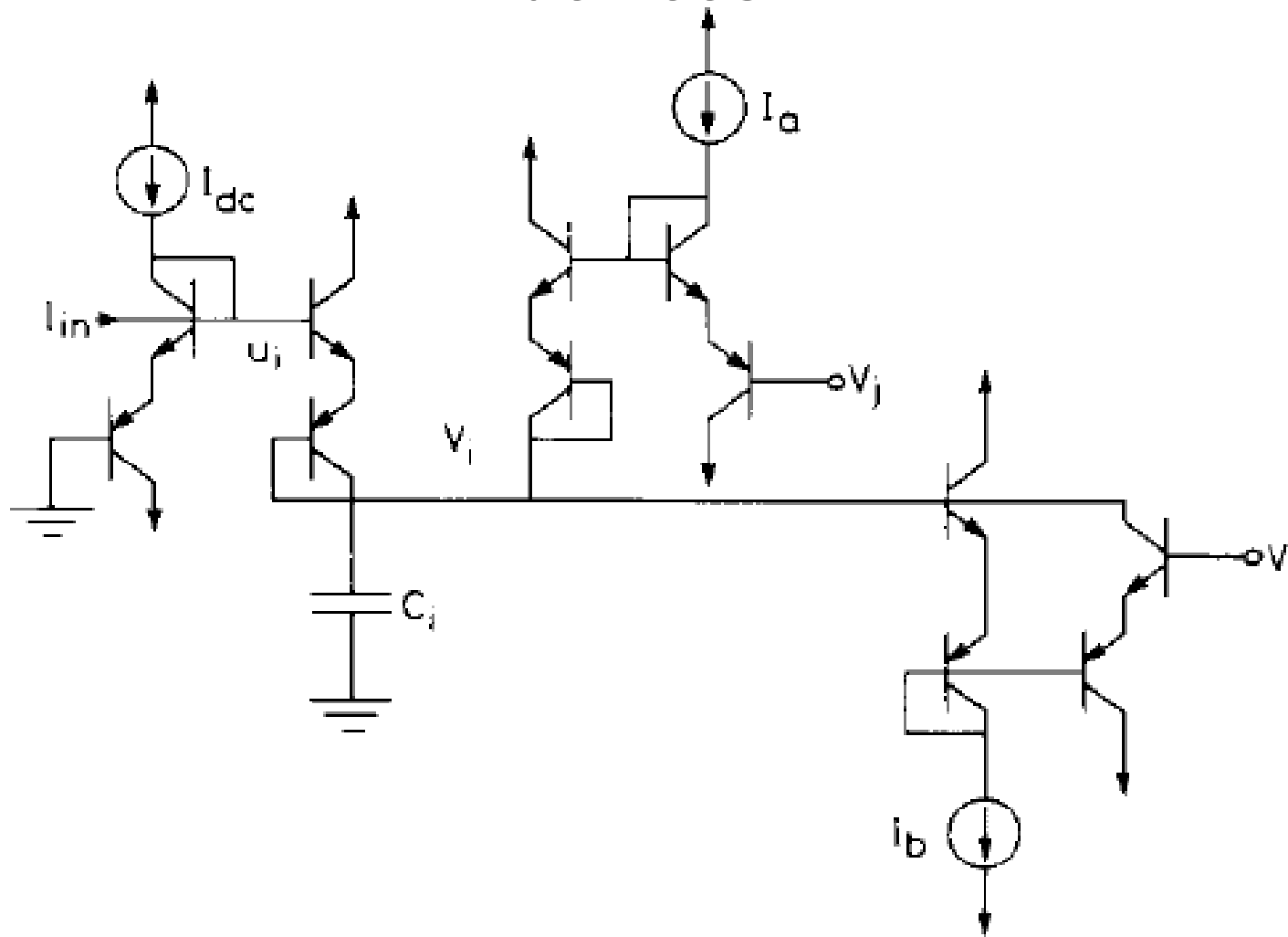The Bernoulli cell using complementary devices



A biquad filter: 2 Bernoulli cells and a mirror linking them

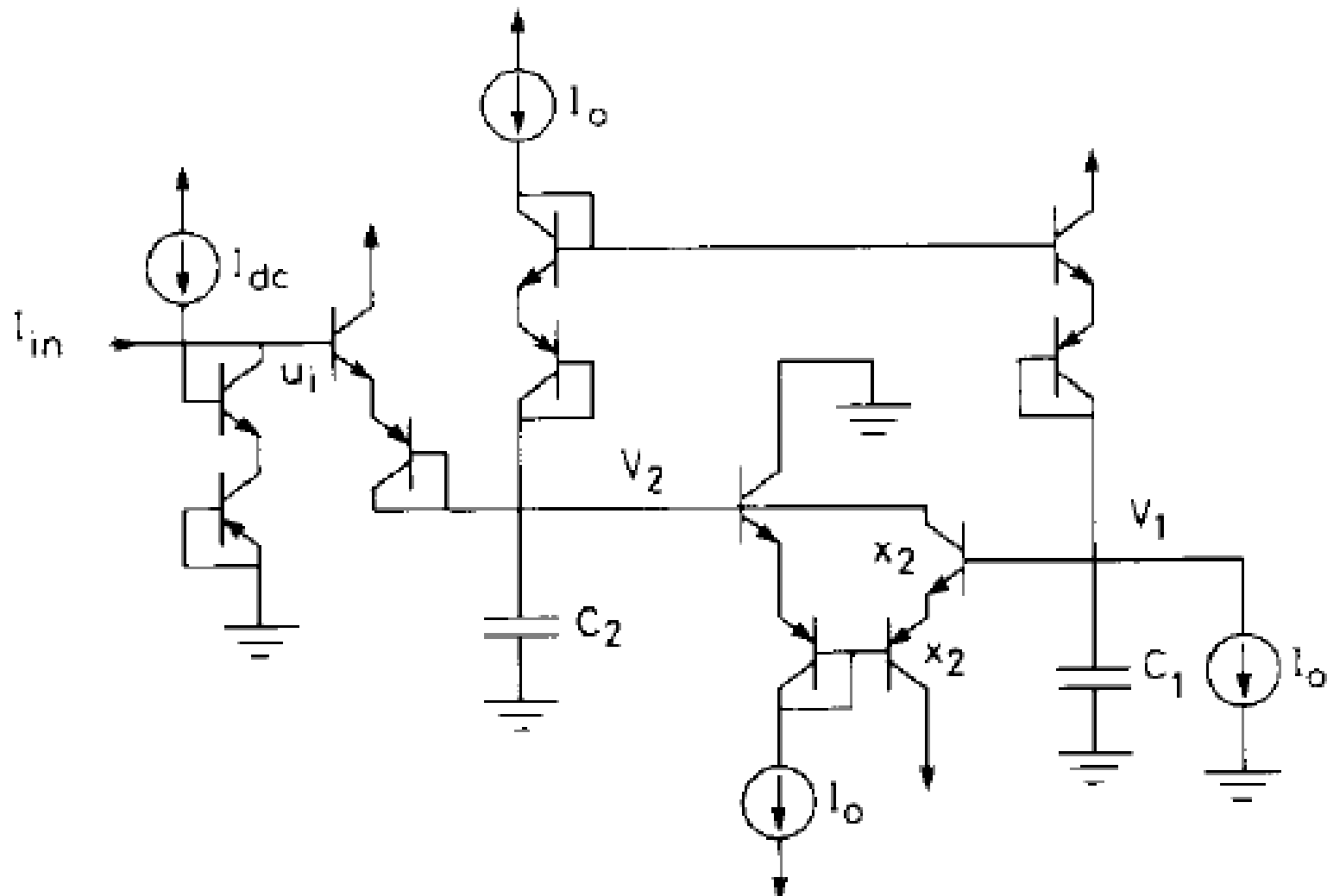

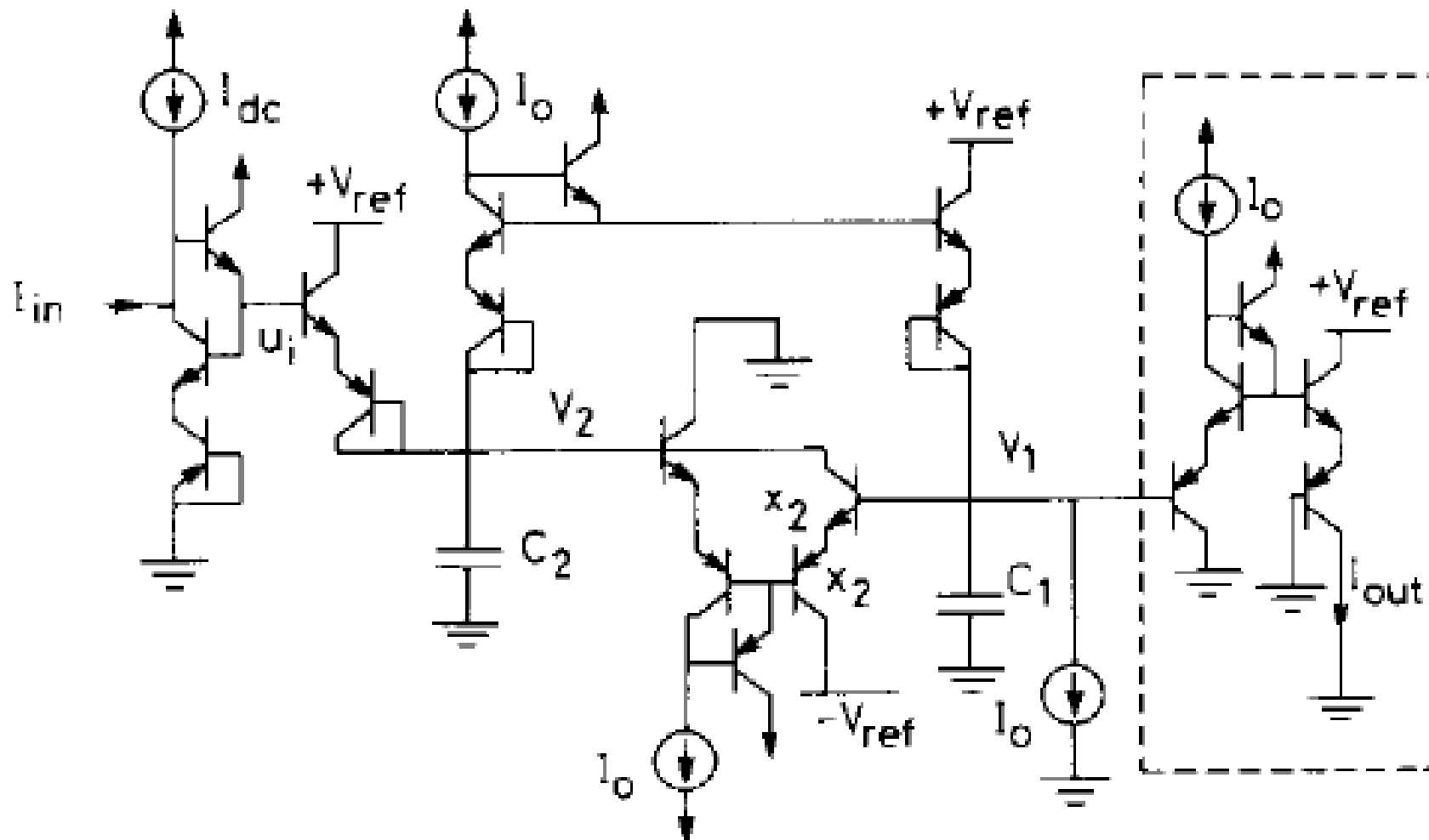


Fig. 7 Complete second-order lowpass-filter schematic diagram

Example of implementing the state variable output equation

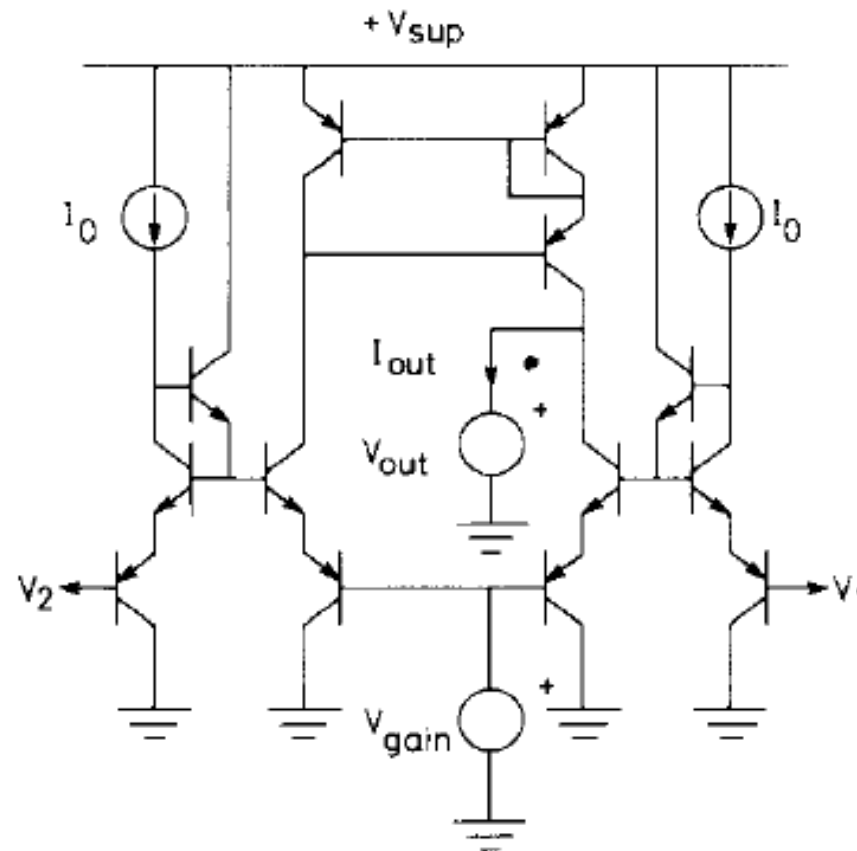


Fig. 8 Output-circuit schematic diagram for converting the circuit of Fig 7 to a bandpass filter

Implementations tend to have lower cutoff than designed

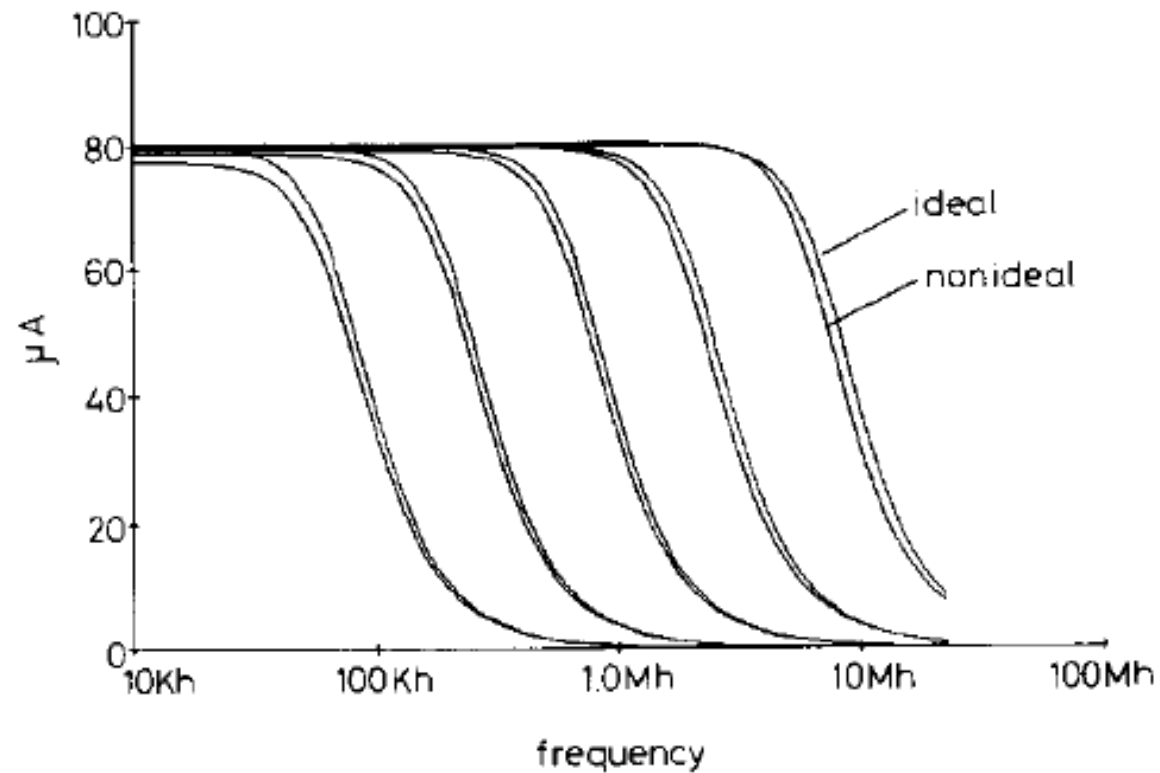


Fig. 9 *Second-order Butterworth lowpass log-filter characteristics*

Observe the current is not distorted!

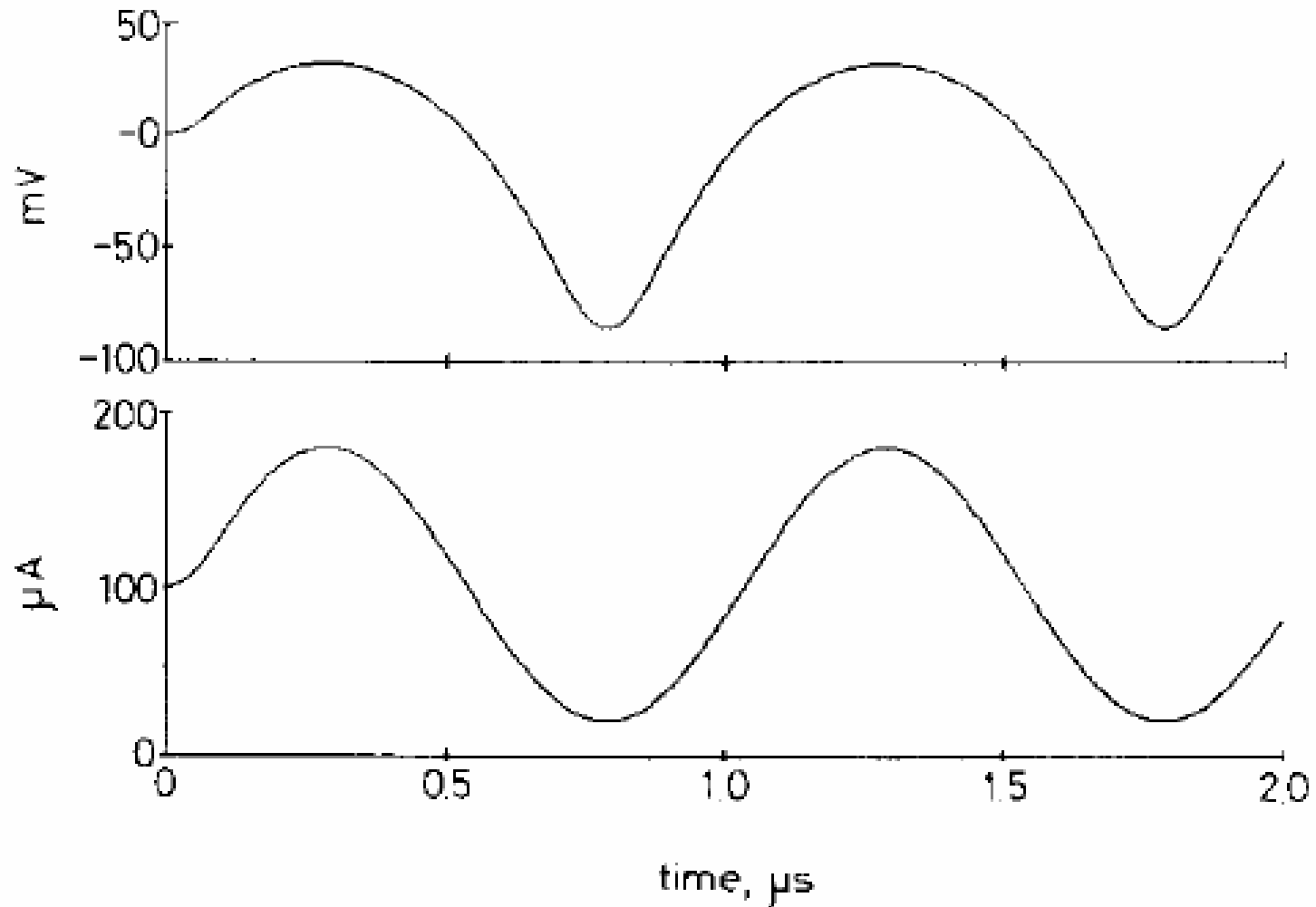


Fig. 10 *Zero-state response of second-order Butterworth filter*

Implementation tends to have higher Q than designed


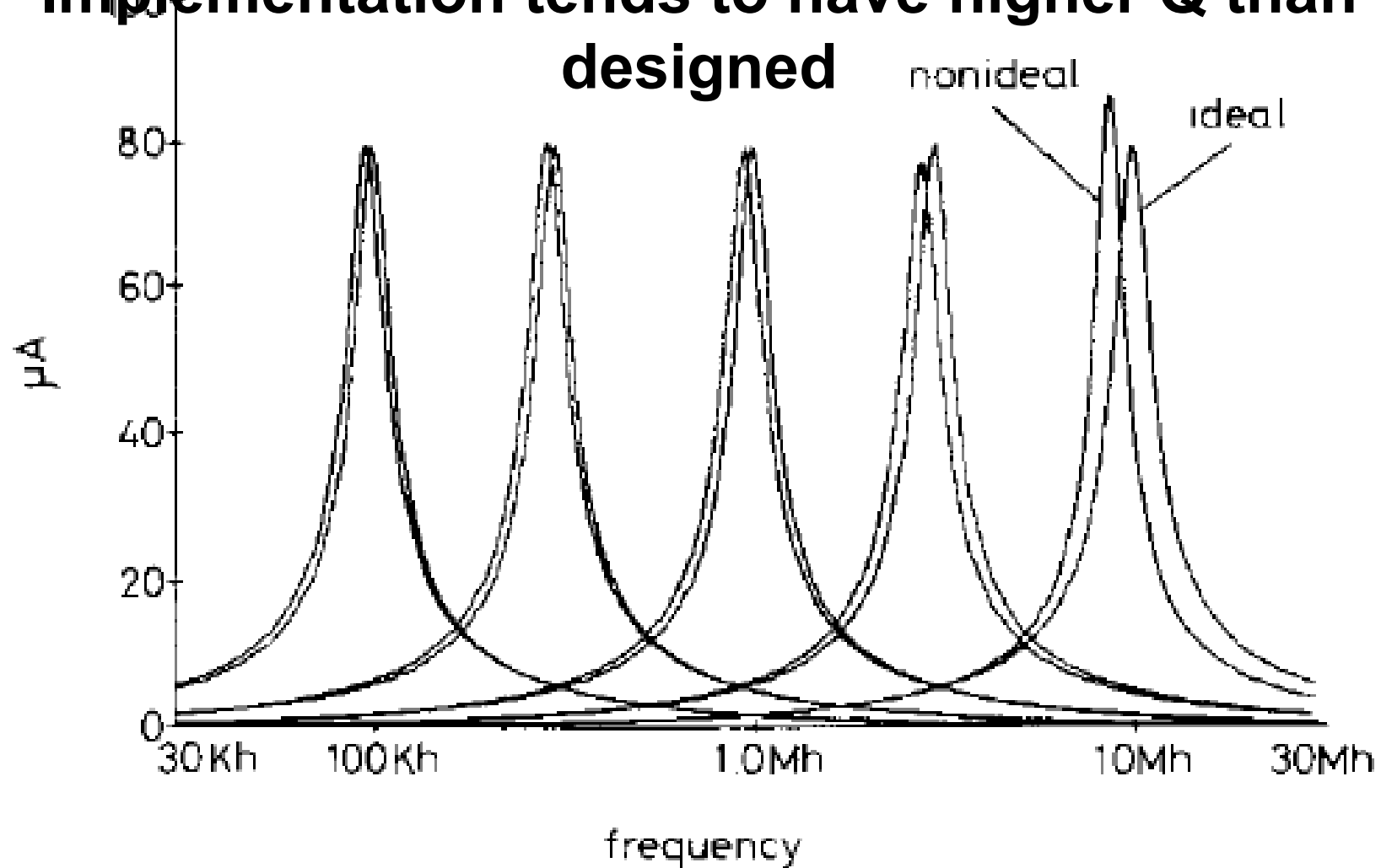


Fig. 11 *Bandpass log filter ($Q = 5$) characteristics*

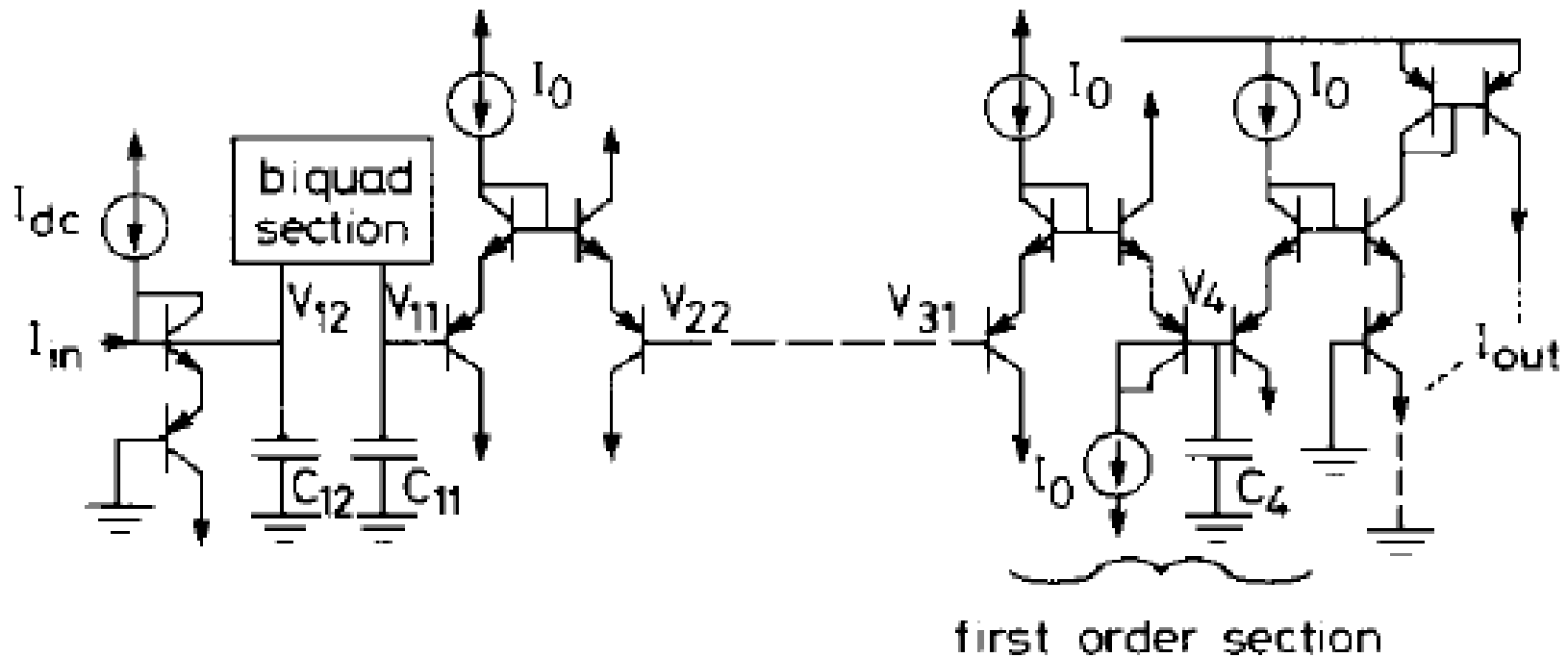Realising high order filters feedback not shown



Note the linear Y scale, and the innacuracy in pole placement


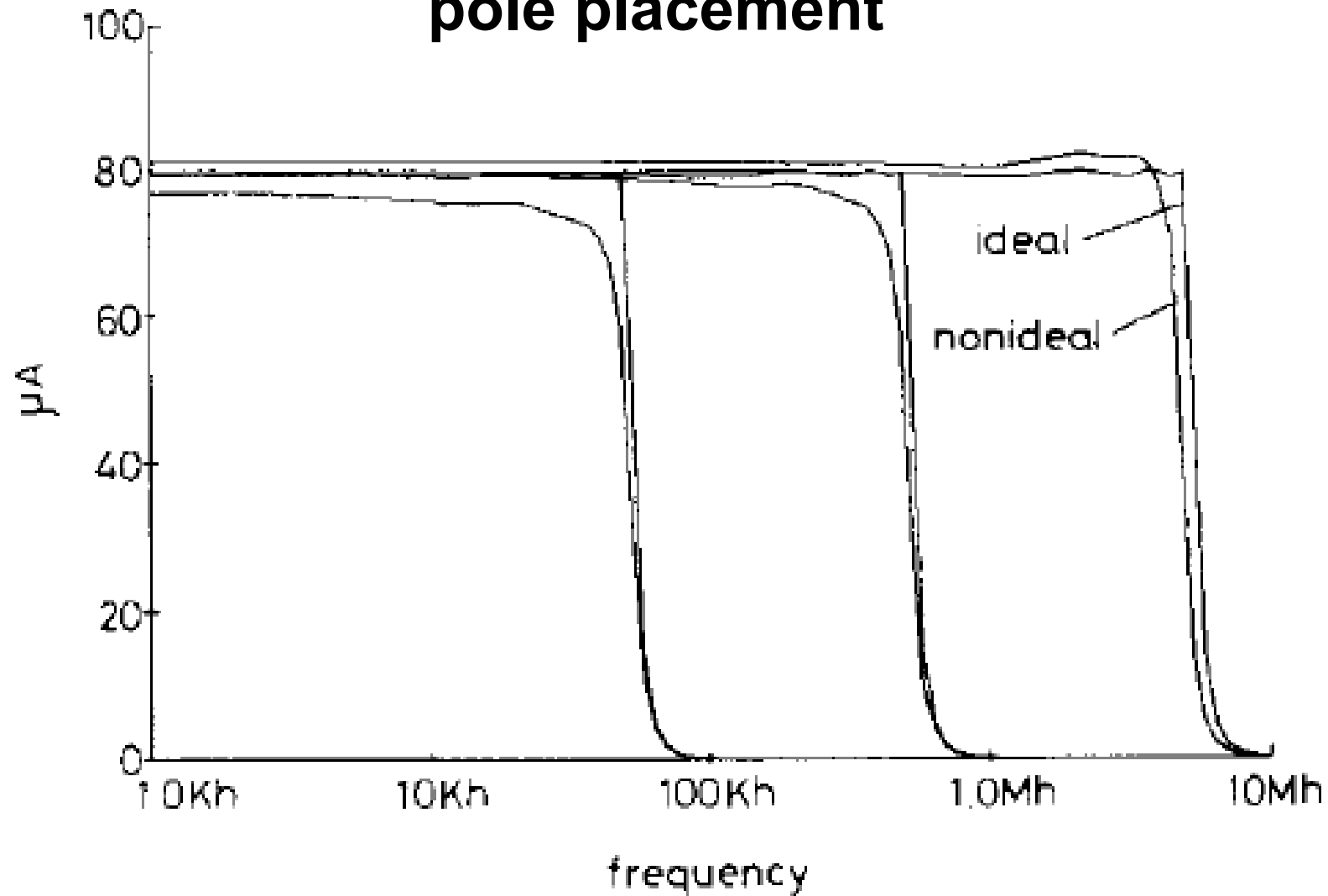


Fig. 14 *Seventh-order Chebychev log-filter characteristics*

ELIN (“E+” cell) Coupling structure

INPUT current = exp (V difference)

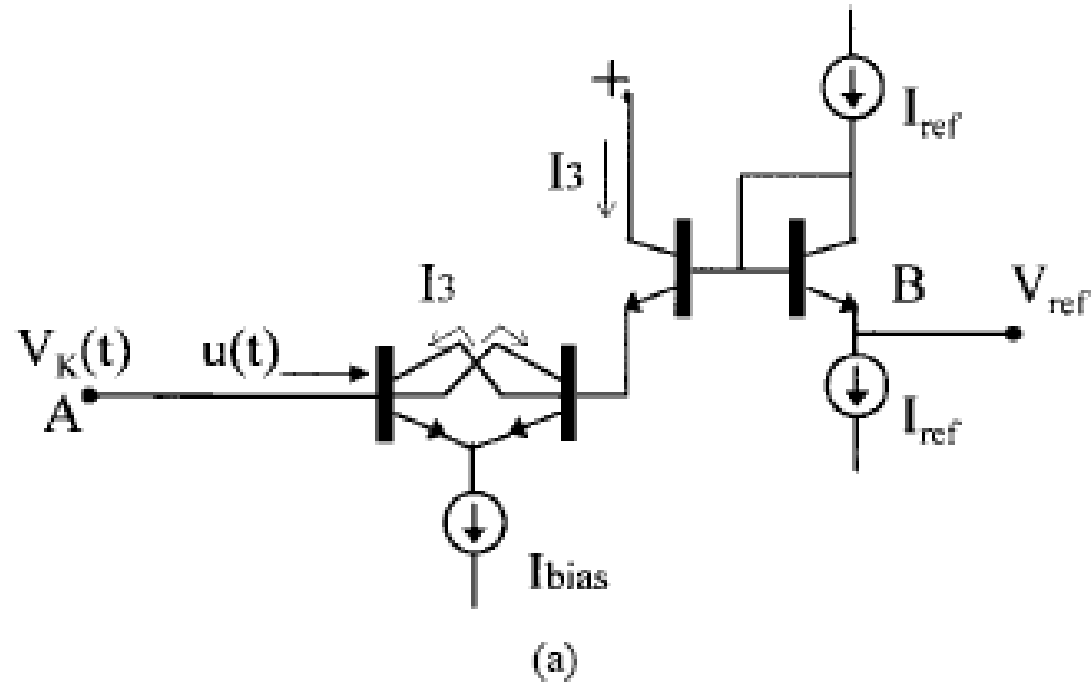

$$u(t) = I_{\text{ref}} \exp[(V_{\text{ref}} - V_K(t))/V_T].$$

Example of Biquad analysis

